



Turn to the Experts.™

VFD Basic

Chee Nee Bong

Oct 2012

VFD BASIC



Turn to the Experts.™

Overview

Fundamentals

Centrifugal operation

Affinity Laws

Tower Reset & ARI

AC Motor

Electrical Basic

VFD Components & Basic Theory


Formulas

VFD Basics

Fundamentals of Centrifugal Operation



Turn to the Experts.™

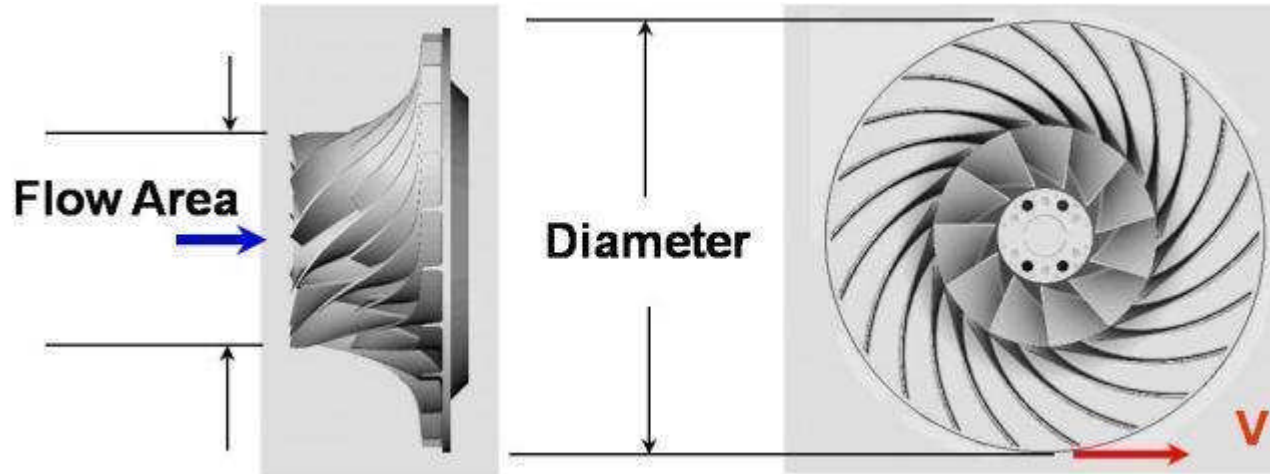

The basic physics are the same for centrifugal pumps, fans and compressors

Flow ~ V

To increase flow, increase flow area or rotor speed

Lift ~ V²

To increase lift, increase diameter or rotor speed

Power ~ Flow x Lift ~ V³

With constant flow and reduced lift, reduce speed to reduce power


VFD BASIC



Turn to the Experts™


Affinity Laws for Centrifugal Loads [Fans and Pumps (no static head)]

Flow ~ Speed

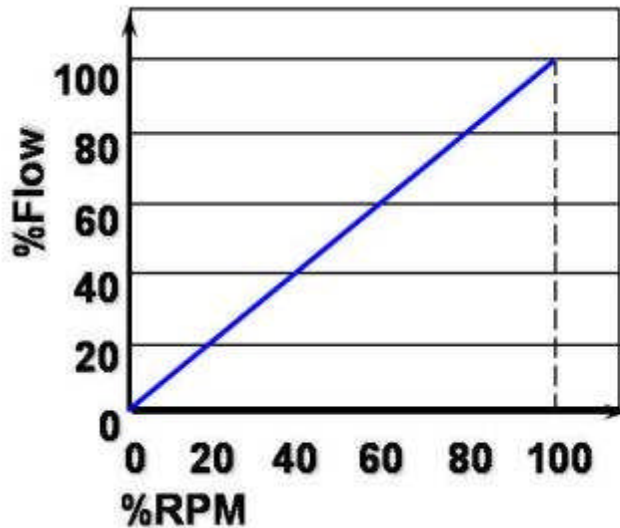


Capacity drops as we slow down the compressor

Lift ~ Speed²

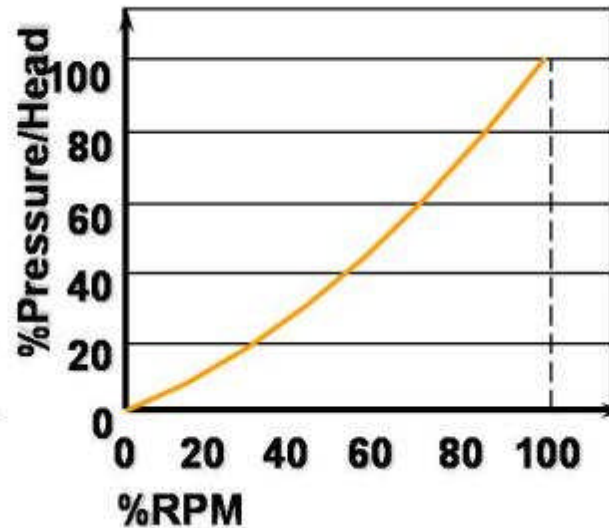

Lift drops off faster as we slow down the compressor

Power ~ Speed³

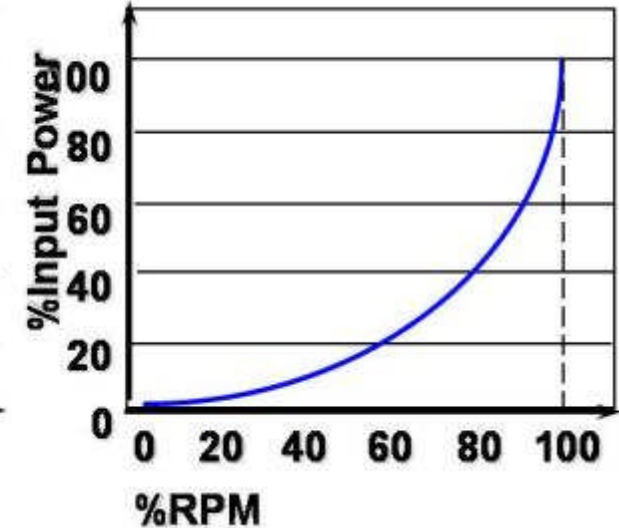

But Power Usage drops even faster!

VFD BASIC



Turn to the Experts.™

The Affinity Laws

Flow is proportional to shaft speed

Head is proportional to square of shaft speed

Power is proportional to cube of shaft speed

VFDs take advantage of the affinity laws which state

“As the speed of a centrifugal load decreases, the horsepower requirement will decrease with the cube of the speed.”

Numeric Description of The Affinity Laws

Speed	Flow	Required Power
100%	100%	100%
90%	90%	73%
80%	80%	50%
70%	70%	34%
60%	60%	22%
50%	50%	13%
40%	40%	6%
30%	30%	3%

VFD BASIC



Turn to the Experts™

How does speed affect power ?

19XRV is taking advantage of the use of Tower Water Reset (set point for leaving condenser water)

Critical with 19XRV (VFD) chillers

Tower water temperature goes down, compressor speed is reduced

$\text{Speed}^3 = \text{Power}$

$\text{Speed} = \text{Flow}$



VFD BASIC



Turn to the Experts™

ARI condition: Old vs. New

**TABLE 3. - ENTERING CONDENSER FLUID TEMPERATURES AT PART LOAD
I-P SYSTEM**

% LOAD	1992 STANDARD			1998 STANDARD		
	WC °F ECWT	AC °F EDB	EC °F EWB	WC °F ECWT	AC °F EDB	EC °F EWB
100%	85	95	75	85	95	75
75%	78.75	85	68.75	75	80	68.75
50%	72.5	75	62.5	65	65	62.5
25%	66.25	65	56.25	65	55	56.25

WC = water-cooled

AC = air-cooled


EC = evaporative cooled

ECWT = entering condenser water temperature

EDB = entering air dry bulb temperature

EWB = entering air wet bulb temperature

New ARI 550/590-1998

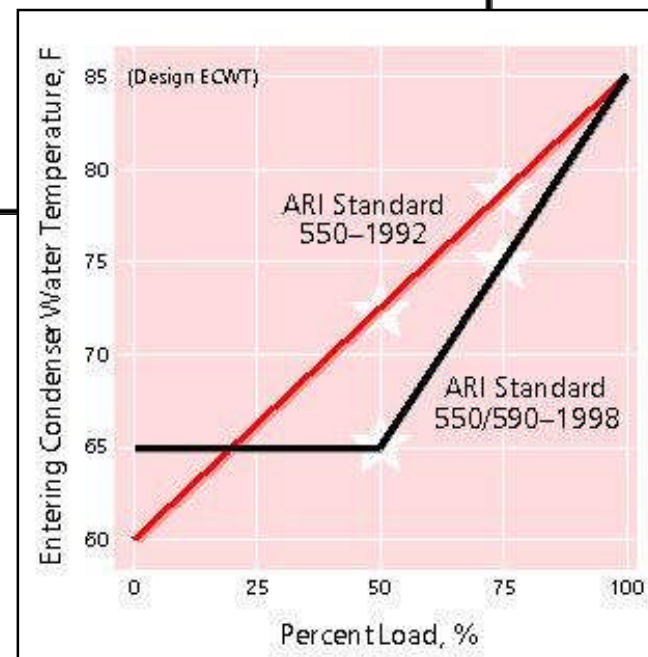

VFD BASIC



Turn to the Experts.™

Tower Reset & ARI Condition

100% load, 55~44°F Chilled Water, 3 GPM @ 85°F Tower water

For each 10% drop of load, the tower water must drop 4°F from design. Therefore, at 75% load, the tower water should be @ 75°F

So...Why Tower Water Reset at Part Load Necessary ?
When mass flow is reduced, the ability to produce lift decreases.

The guide vane angle changes, thereby reducing the lift ability. Compressor will surge




VFD BASIC

VFD applied savings



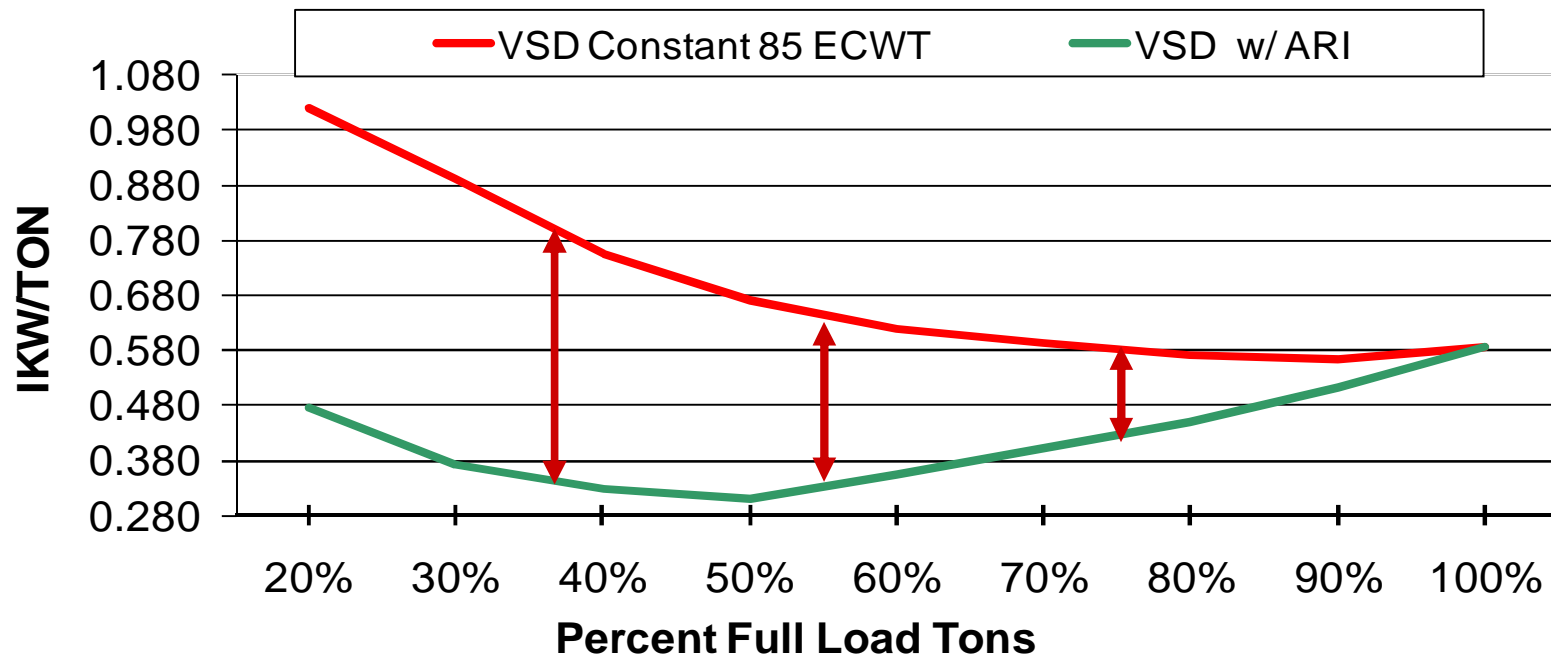Variable Speed Centrifugals with Constant vs. ARI Condenser Water Temperatures



A VSD chiller reduces KW-HR consumption


VFD BASIC



Turn to the Experts.™

Centrifugal: VFD vs. Constant Speed

VFD vs. Constant Speed Centrifugal

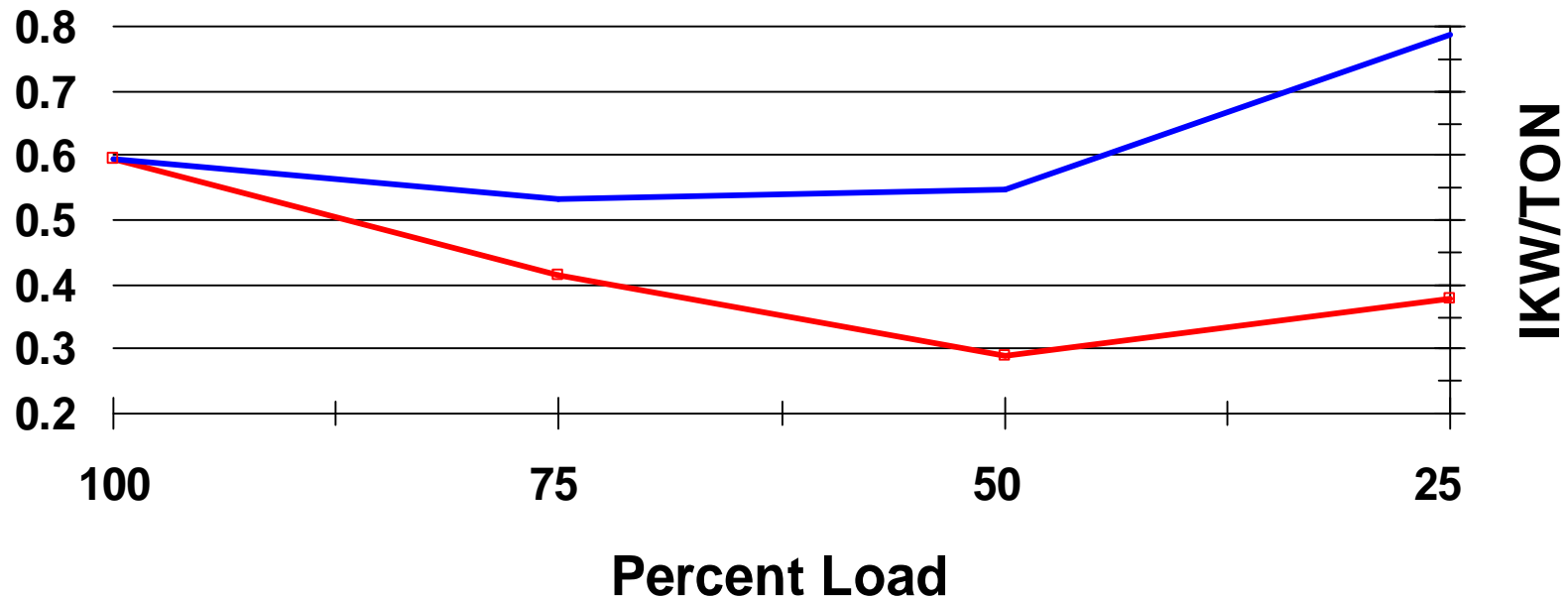

Primary function of VFD is to improve part load efficiency

— 19XR @ Constant Speed on ARI

— 19XRV on ARI

VFD BASIC

AC Motor



Turn to the Experts.™

AC Induction Motor

Power by Electromagnetic Induction

How does this work ?



VFD BASIC



Turn to the Experts.™

AC Motor


Magnets – material that produces magnetic field. Unlike poles attract, like poles repel

Magnetic field – region around magnet or electric current where there is a magnetic force within the region

Magnetic flux – number of magnetic lines of force leaving or entering the poles of a magnet

Flux Density -- # flux lines per unit area. The Greater flux density, the greater field intensity.

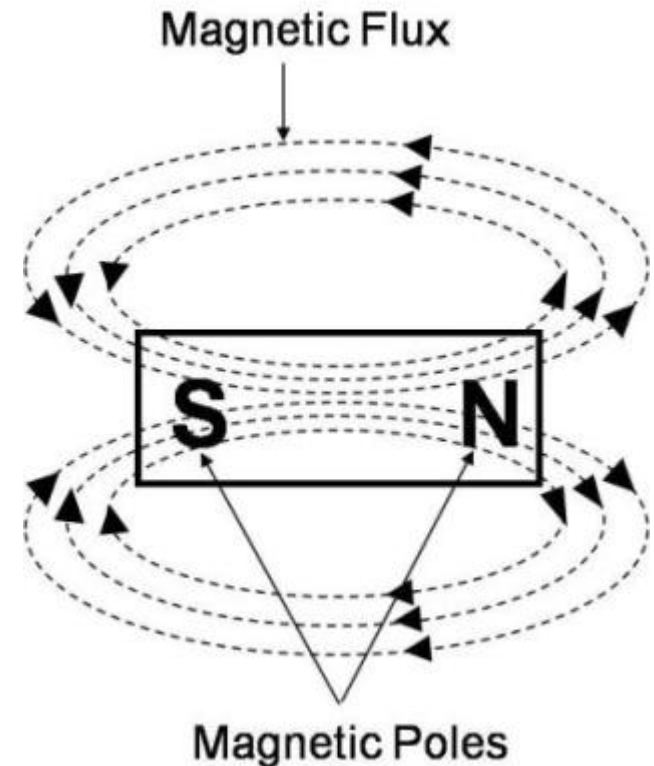Intensity of magnetic field is related to magnetic force



VFD BASIC

AC Motor



Turn to the Experts.™

Electricity and Magnetism


Electric current is generated in a wire by moving current through a magnetic field

Electric current produces magnetic field

Electromagnet creates magnetic field from electric current moving through the coils

***The higher the number of turns in a coil, the stronger the magnetic field that is developed around it.*

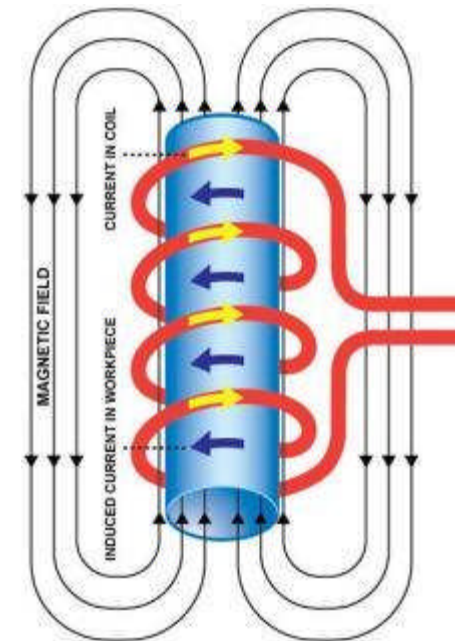***With fixed number of coil, magnetic field strength is directly proportional to the amount of current flowing within the coil*



VFD BASIC



Turn to the Experts™

AC Motor

What are the characteristics of magnetic lines of force ? Magnetic lines of force are

- Continuous & always form closed loops

- Do not cross one another

- Parallel magnetic lines travelling in same direction repel one another

- Parallel magnetic lines travelling in opposite directions unite with each other to form single lines

- Magnetic lines existing between two unlike poles causes the poles to pull together

- Pass through all materials, both magnetic and non-magnetic

- Leave magnetic material at right angles to the surface

VFD BASIC



Turn to the Experts.™

AC Motor

AC motor operates by creating magnetic field that rotates around rotor


There stator and rotor are not directly connected

Energized stator creates rotating magnetic field around rotor bar


Magnetic field in Rotor bar interact with magnetic field of stator causing both to rotate

Induced voltage causes current flow in rotor bar

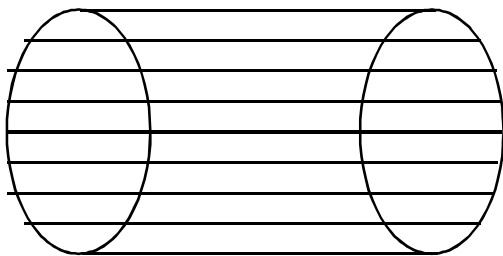Amount of induced voltage depends on flux and speed



Squirrel Cage Rotor (Motor)


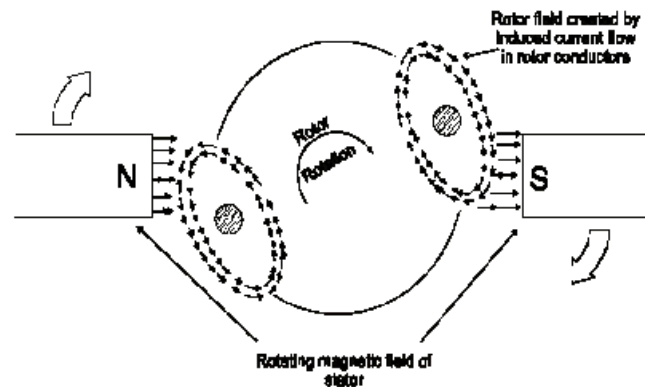


VFD BASIC


Rotating Magnetic Field




Turn to the Experts™

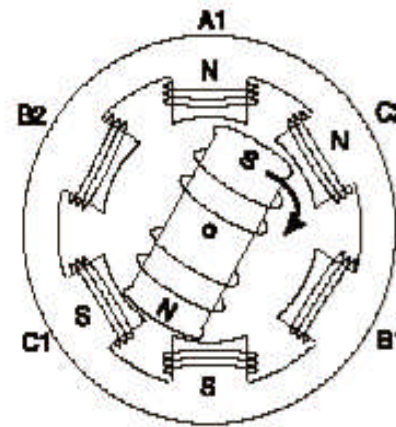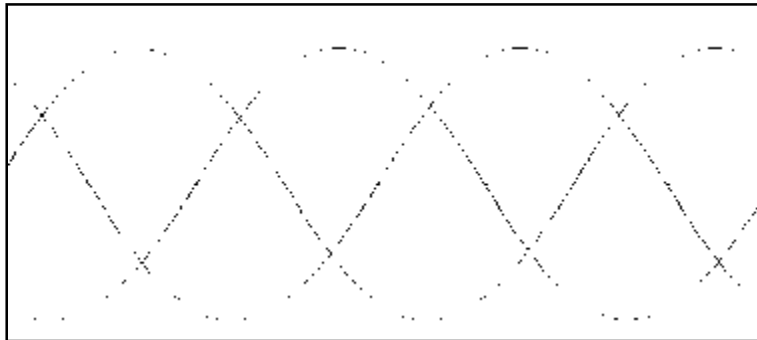


TIME 1

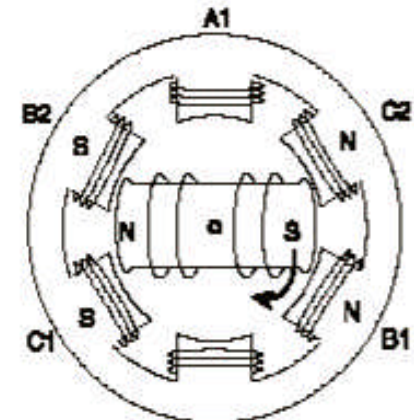

TIME 2

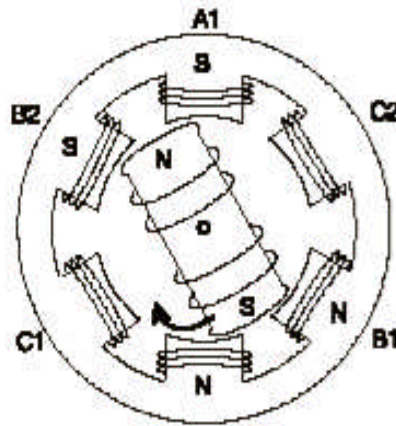

TIME 3

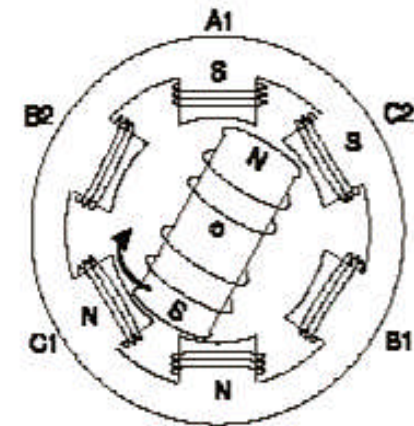

TIME 4

By progressively changing stator pole polarity a rotating magnetic field is created

VFD BASIC



Turn to the Experts™

AC Motor

Speed (RPM) – number revolution per unit time frame

Torque (ft.lb) – turning power of motor

Horsepower (hp) – combination of both torque and speed

Slip = Speed of synchronous speed (rotating magnetic field) – Rotor Speed, difference between synchronous speed and actual speed

$$\begin{aligned} \text{Motor Base Speed (RPM)} &= \text{Synchronous Speed} - \text{Slip} \\ &= \frac{120 \times \text{Applied Frequency}}{\# \text{ Poles per Phase}} - \text{Slip} \end{aligned}$$

Slip is necessary to create torque

Frequency is the variable in the above formula


Thus, we use variable frequency drives (VFD) to control speed of motor

VFD BASIC



Turn to the Experts.™

Synchronous Speed

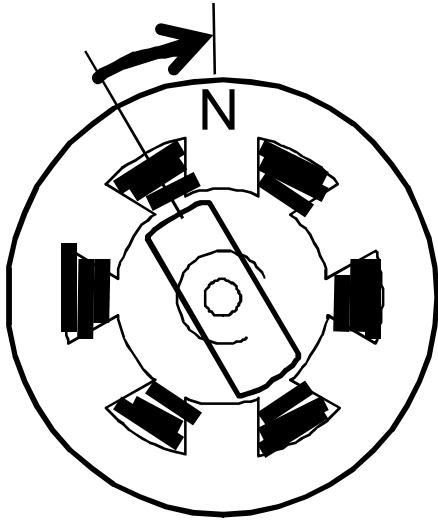

$$\text{Sync Speed} = \frac{120 \times \text{Applied Frequency}}{\text{Number of Poles Per Phase}}$$

Example for 2 poles motor:

At 60 Hz: $(120 \times 60\text{Hz})/2 = 3600\text{RPM}$

At 30 Hz: $(120 \times 30\text{Hz})/2 = 1800\text{RPM}$

VFD BASIC



Turn to the Experts™


Motor Base Speed (Nameplate Speed)

$$\text{Motor Base Speed (RPM)} = \frac{120 \times \text{Applied Frequency}}{\text{Number of Poles Per Phase}} - \text{Slip}$$

$$= \frac{120 \times 60 \text{ Hz}}{2} - \text{Slip}$$

$$= 3600 \text{ RPM} - 40 \text{ RPM}$$

$$= 3560 \text{ RPM}$$

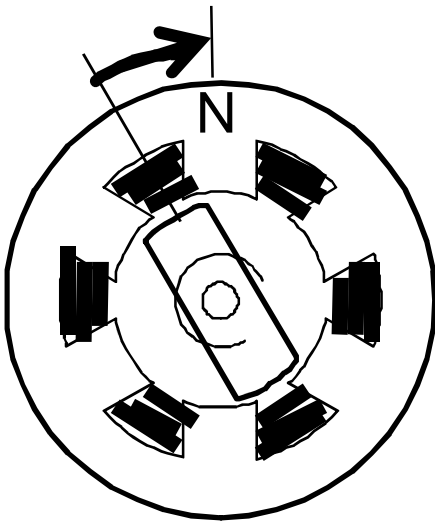

VFD BASIC

AC Motor



Turn to the Experts.™

Rotor

Connected to External device

Transfer Electrical energy into mechanical

Motor Housing


Stator Windings

Input connected to these windings

Current flows through and induces voltage on Rotor

Motor Bearing

Position Stator in Place

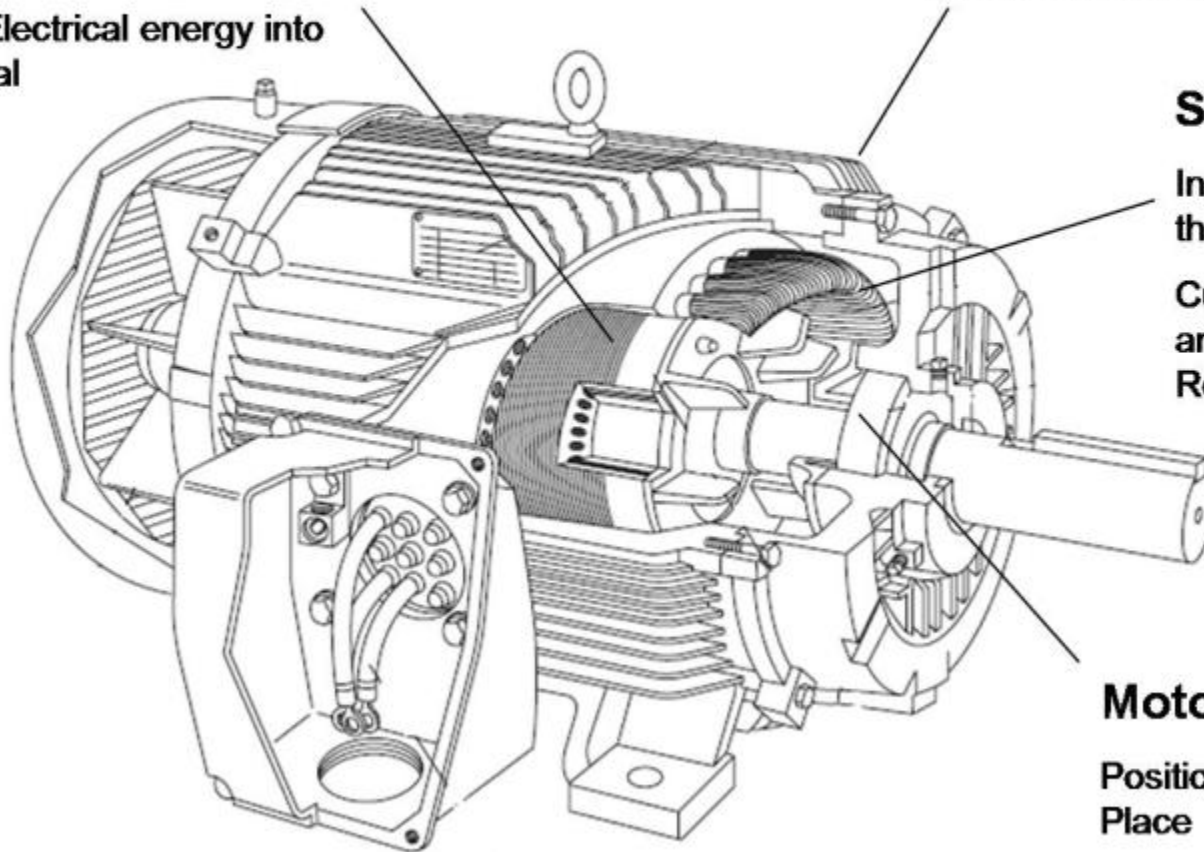

VFD BASIC




Turn to the Experts™

NEMA – Rotor Characteristics

National Electrical Manufacturers Association

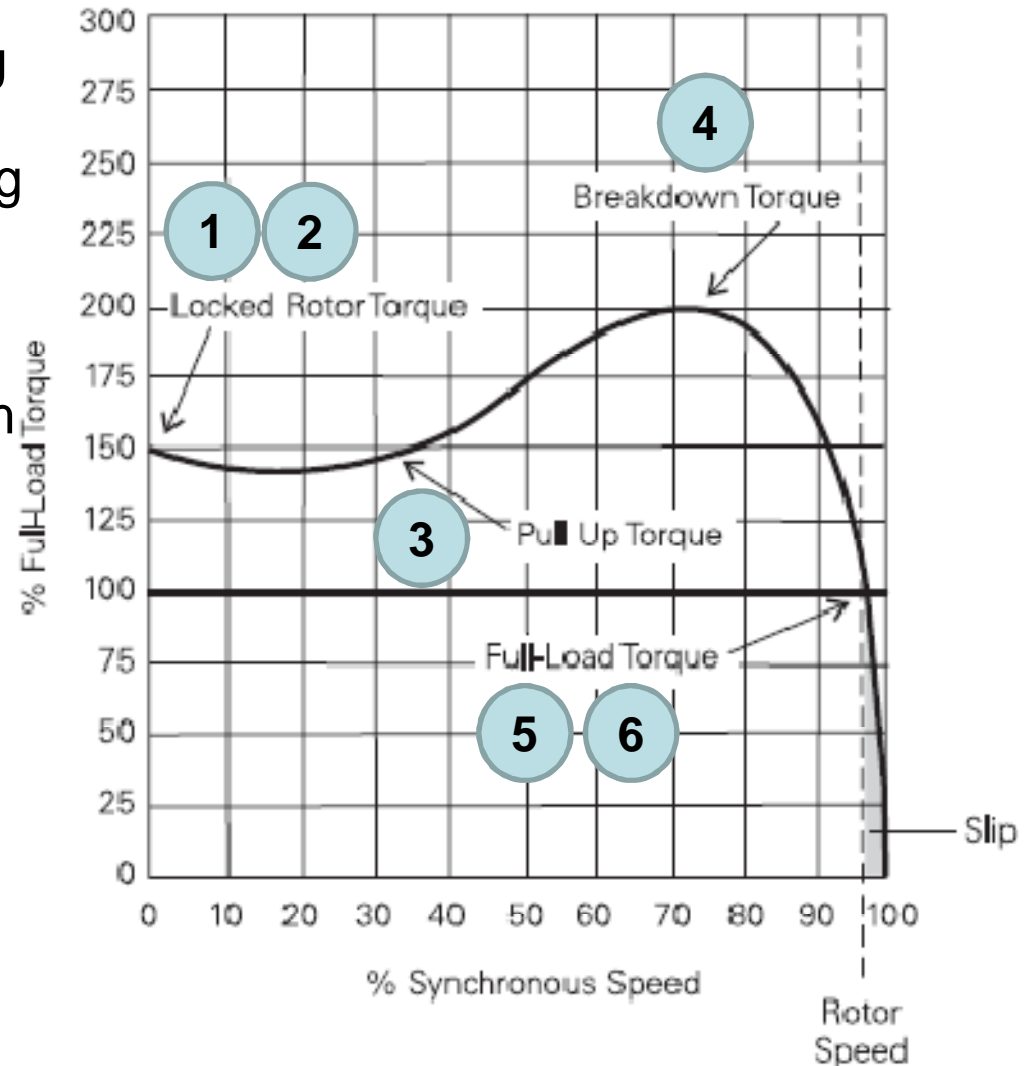1. Locked Rotor Torque – starting torque
2. Locked Rotor Current – starting current
3. Pull Up Torque – acceleration from start to breakdown torque
4. Breakdown Torque – maximum torque without abrupt loss of speed
5. Full Load Torque – motor at rated voltage, frequency, load
6. Full Load Current – supply line current at rated voltage, frequency, load



VFD BASIC



Turn to the Experts™

NEMA – Motor Type Classifications

National Electrical Manufacturers Association

Design A – No Limit on LRA, used at higher LRA for low slip & higher efficiency, unstable at high load condition

Design B -- most common and most suitable for AC drives, applied in variable torque, constant torque and constant horsepower, good efficiency, low slip

Design C – high starting torque, higher slip, high pull up torque, no use with VFD

Design D – high impact, high starting torque, high inertia load. High LRT, high slip, low efficiency

Speed & Torque – load change affect slip & torque. When Load increase, slip & torque increase, vise versa

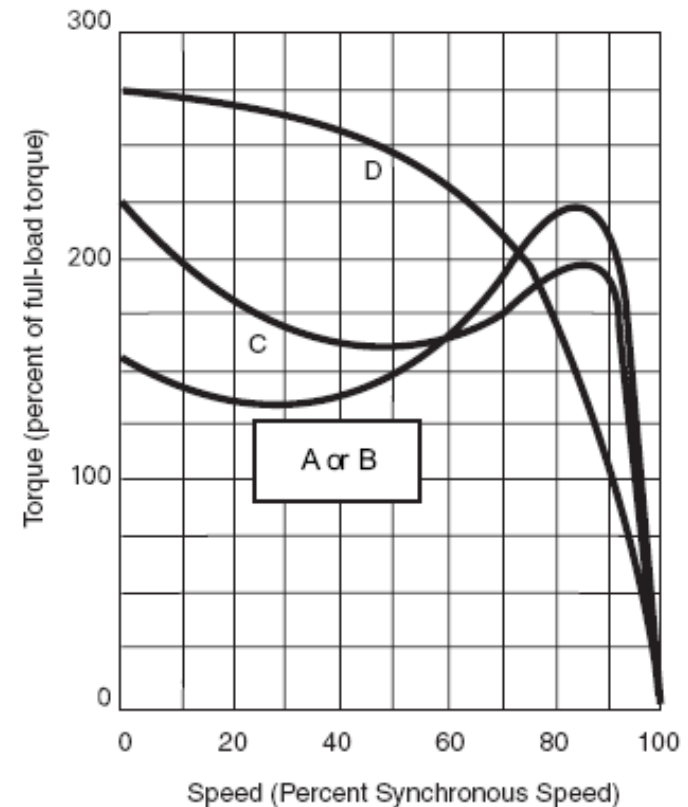


Figure 2-8: Typical Motor Speed Torque Curves

VFD BASIC



Turn to the Experts™

Electrical Basics


Frequency

of complete cycles of an AC signal per second

Measured in Hertz

60HZ – sixty complete cycles per second

$T=1/F=1/60=0.0167$ seconds per cycle

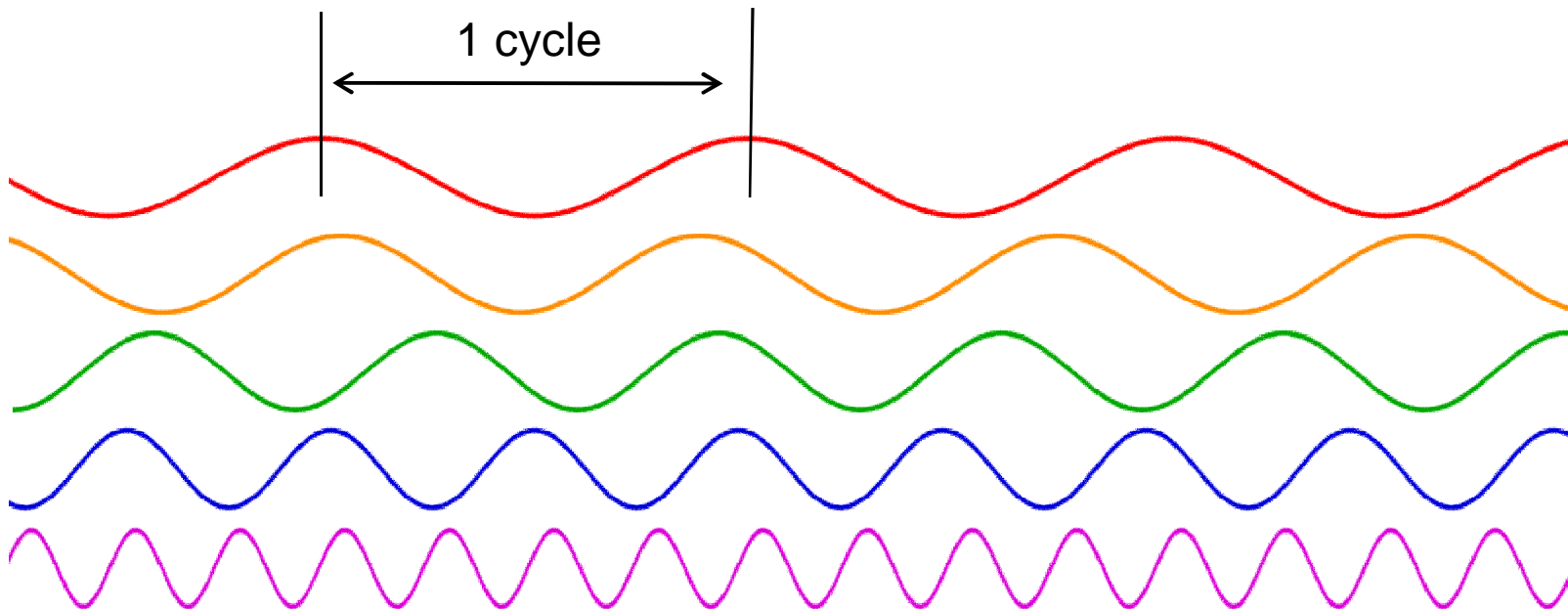


VFD BASIC



Turn to the Experts™

Electrical Basics

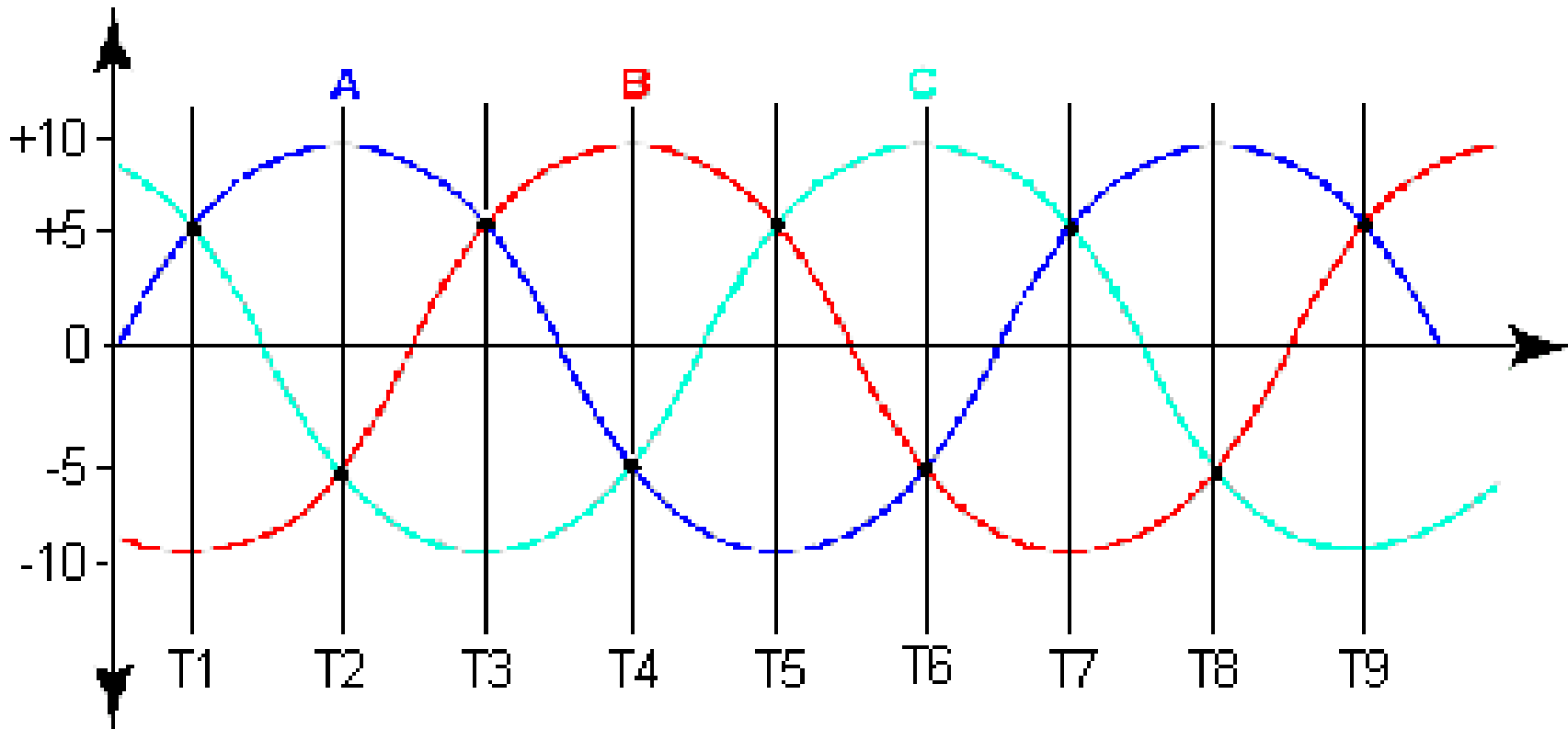A three phase power supply is made up of three separate cycles of power that intersect the other two phases four times every 360 electrical degrees.




VFD BASIC



Turn to the Experts™

Electrical Basics

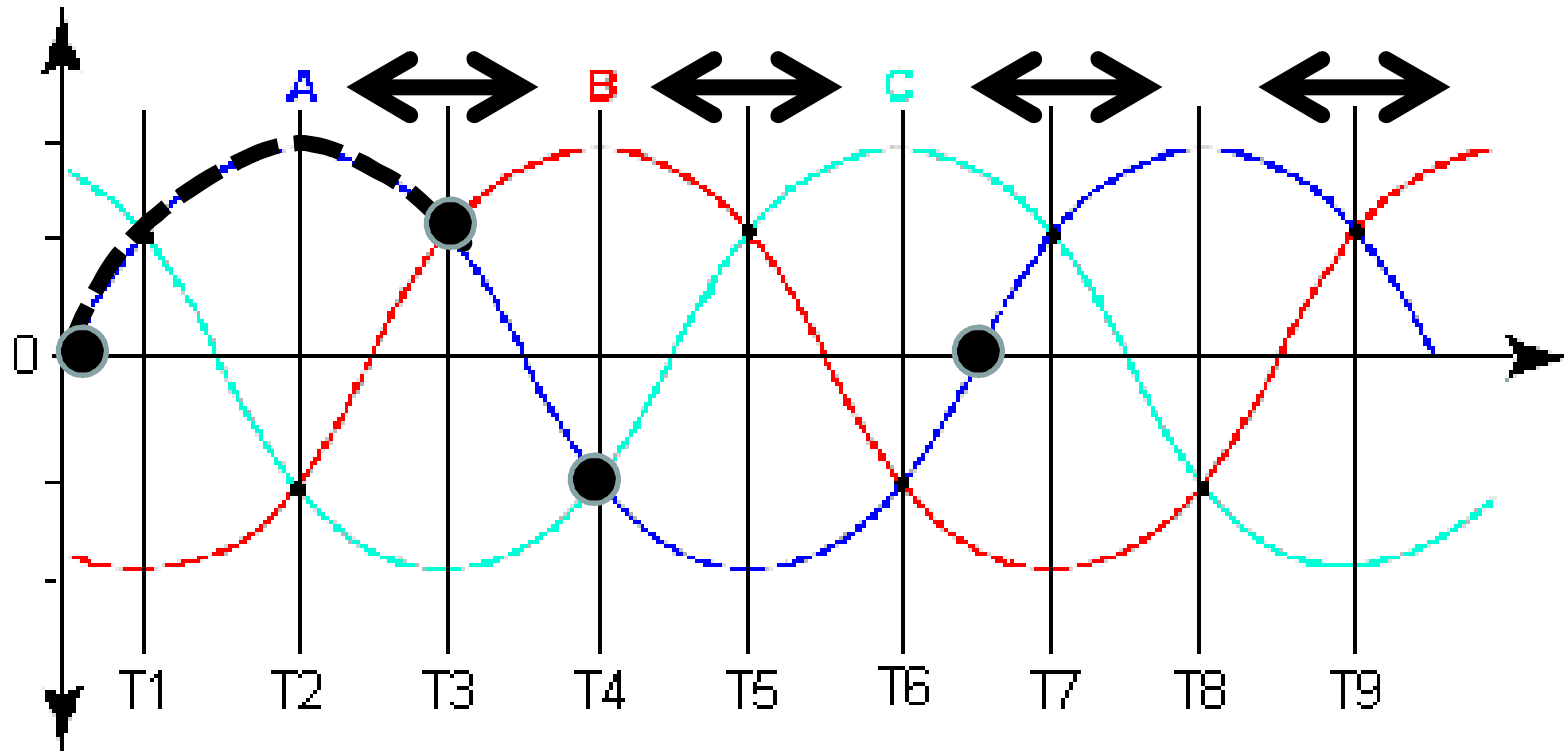

Each phase of power is separated by 120 electrical degrees

VFD BASIC




Turn to the Experts™

Electrical Basics

The Peak voltage is here

RMS Voltage is here

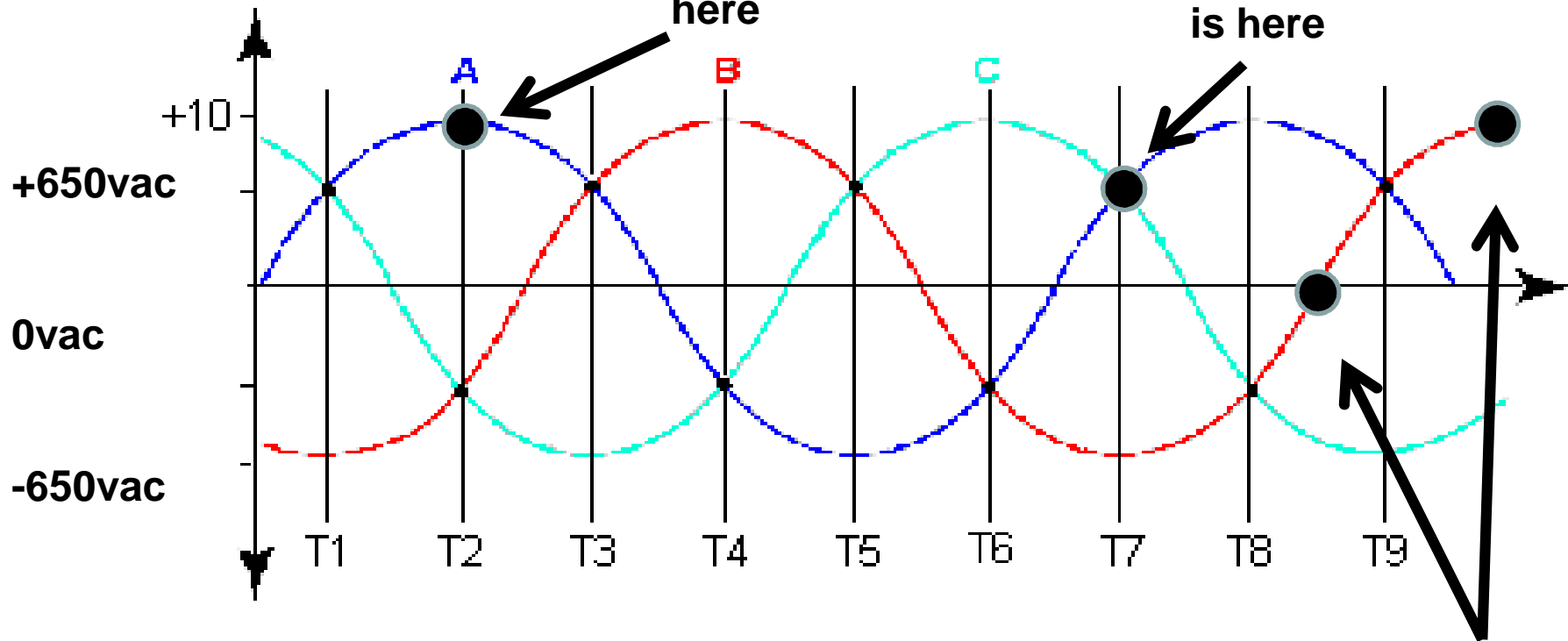

The RMS Voltage is the average of the voltage from the 0 axis to the peak of the sine wave for a particular phase which is the value you will read with your volt meter.


For example: a 460vac RMS measurement will have a peak voltage of 650vac
RMS Measurement is $\times 1.414 = 650\text{vac}$

VFD BASIC



Turn to the Experts™

Electrical Basic: Kirchoff's Current Law

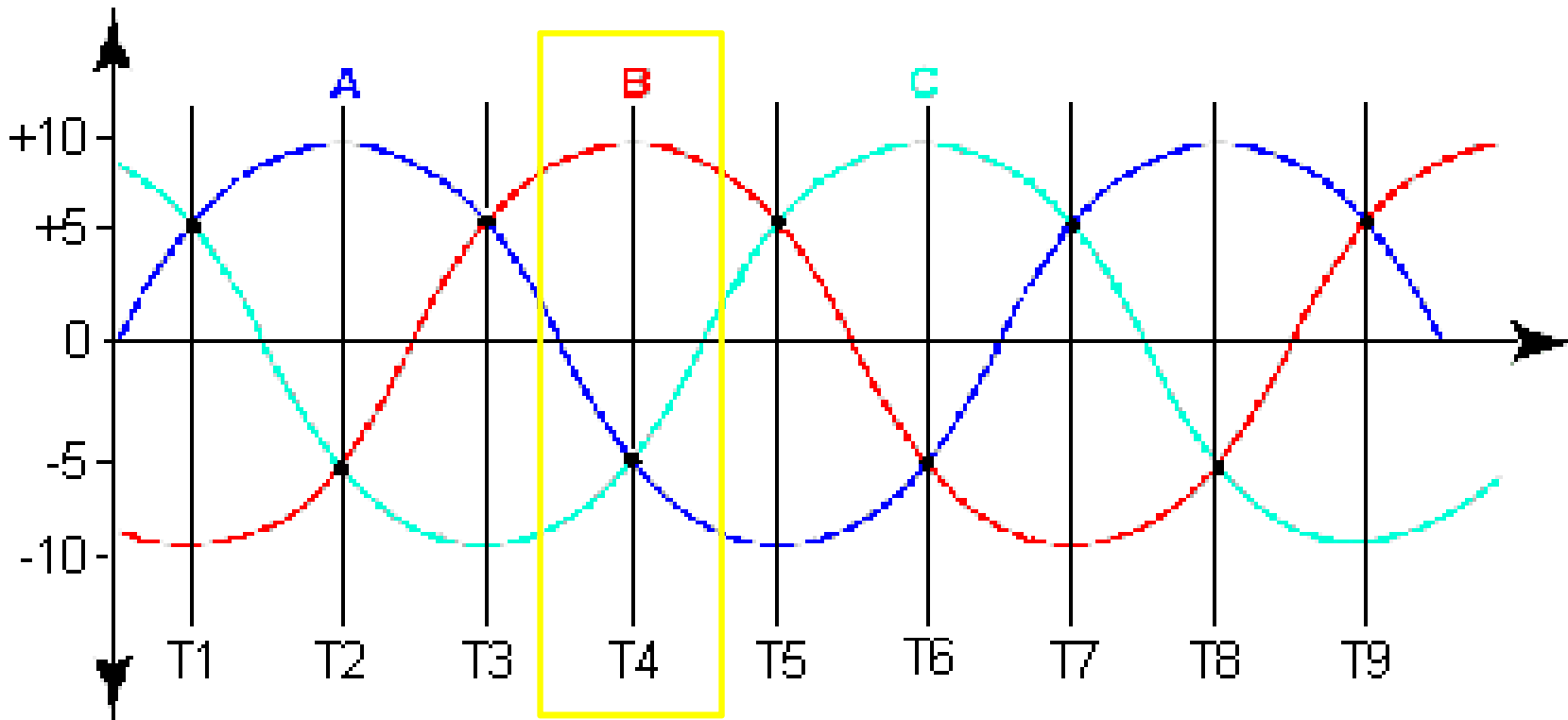

Kirchoff's current law – phase sum of all currents in/out must equal zero

Example:

$$A = -5; B = 10, C = -5$$


$$A + B + C = 0$$

VFD BASIC

Electrical Basic: Kirchoff's Current Law



Turn to the Experts™

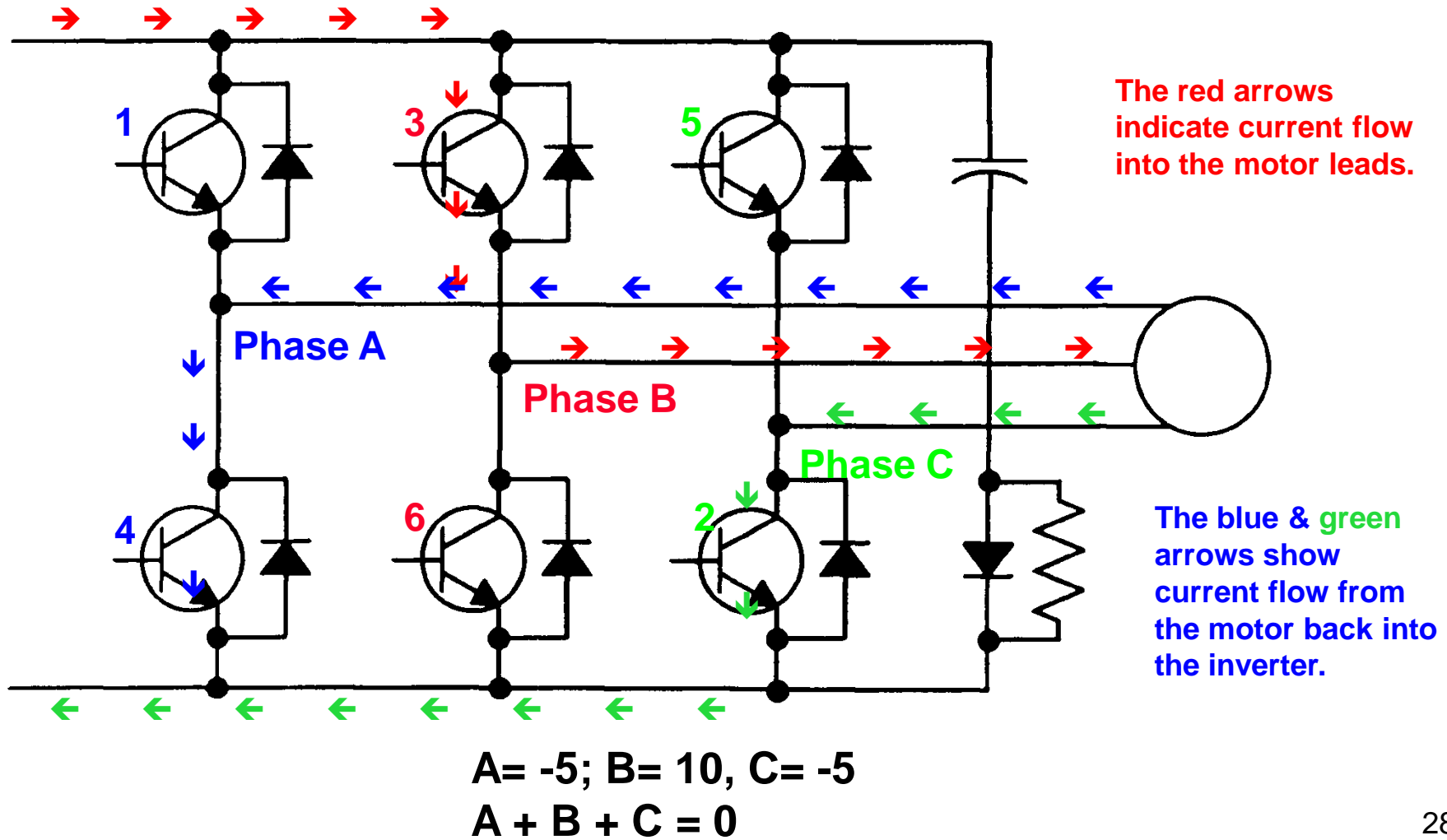

VFD BASIC



Turn to the Experts.™

Electrical Basics -- Methods of Starting

Across the line

Autotransformer Reduced Voltage

Primary Reactor

Part Winding

Wye Delta (Star Delta)

Solid State Reduced Voltage

Variable Frequency Drive



VFD BASIC



Turn to the Experts™

Electrical Basics -- Methods of Starting

Across the line starting


Simplest and least expensive

Motor Locked Rotor Amps drawn directly from line

Inrush can be 6-8 times motor rated FLA

More suitable for low voltage or medium voltage motor

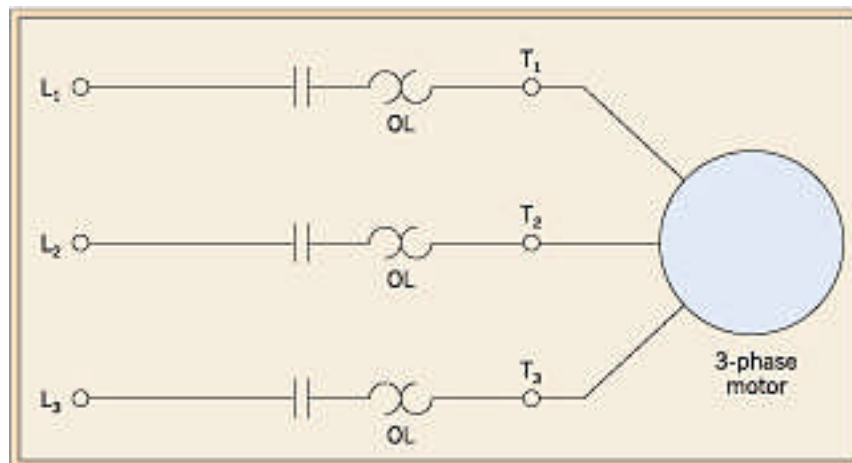On multi compressor chillers, stagger on startup



VFD BASIC



Turn to the Experts.™

Electrical Basics -- Methods of Starting

Autotransformer Reduced Voltage Starting


Reduces inrush line current and motor starting torque by limiting voltage applied to windings

Transformer within starter allow stepped acceleration

Considered a soft start

Start in steps

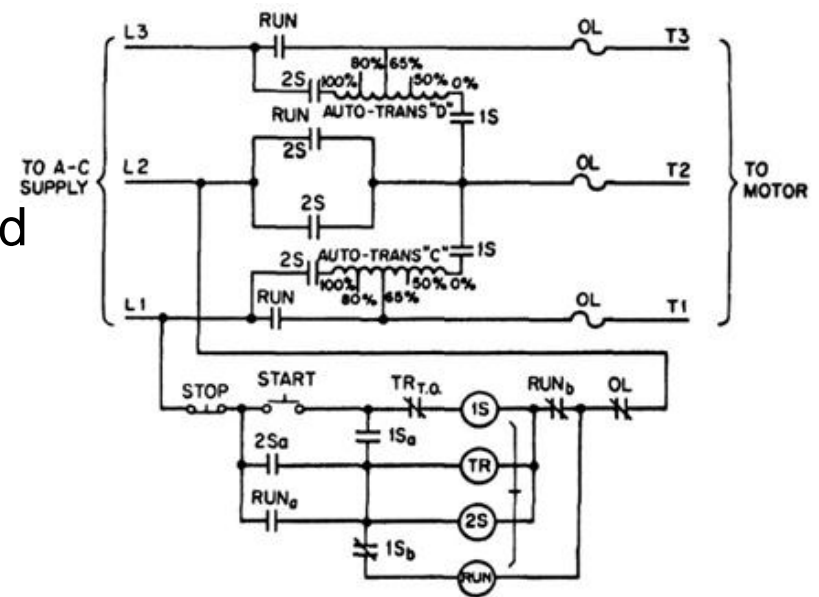Changing line voltage taps in transformer varies current draw from the line, voltage and current, and torque developed by motor



VFD BASIC



Turn to the Experts™

Electrical Basics -- Methods of Starting

Primary Reactor

Like an autotransformer, reduces inrush line current and motor starting torque by limiting voltage applied to windings

Use reactor or resistor instead

More economical for medium voltage

VFD BASIC



Turn to the Experts.™

Electrical Basics -- Methods of Starting

Part Winding

Also produce soft start

Cost effective

Can only be used with part winding motors that have two sets of identical windings for parallel operation

Two step start – energize one winding first

Not used on centrifugal chillers

Mostly used on reciprocal compressors

VFD BASIC

Electrical Basics -- Methods of Starting



Turn to the Experts.™

Wye-Delta

Also called Star-Delta



RediStart MX³

Low Voltage Wye-Delta Motor Control

Reduce inrush line current and motor starting torque by switching motor windings connections

Three contactors and timer change winding configuration from 33% current to full

Low cost compared to reduced voltage type starter

Most common for use with centrifugal chillers under 600 volts

Only use in low voltage application

VFD BASIC



Turn to the Experts.™

Electrical Basics -- Methods of Starting

Solid State

Solid state devices used – SCR (silicon controlled recitifier)

Electronic signal control current flow

Used for both low voltage and medium voltage applications

Programmable soft start



RediStart MX³

Low Voltage Solid State Motor Control

VFD BASIC



Turn to the Experts™

Electrical Basics – Variable Frequency

Vary motor speed by varying frequency of drive signal

Two basic AC drives

- Current Source Drives

- Voltage Source Drives

Voltage source drives

- Names – VFD, ASD, Inverters

- AC-DC-AC topology

- Same basic components –

 - Rectifier/Converter

 - Filter/Capacitors

 - Inverter

VFD BASIC



Turn to the Experts™

Rectifiers/Converter

Converts power from AC to DC using diodes, transistors, or silicon controlled rectifiers (SCR)

VFD using transistor in rectifier is said to have “Active Front End”

One rectifier allows power to pass through when voltage is positive, another allow power to pass through when voltage is negative

3 phase power will have minimum 6 rectifiers

6 pulse means 6 rectifiers

VFD may be 6,12,18, or 24 pulse

VFD BASIC



Turn to the Experts™

Silicon Controlled Rectifiers (SCR)




SCR Inverse Parallel Operation

1 SCR per $\frac{1}{2}$ sign wave

1 negative, 1 positive

3 Phase requires 6 SCRs

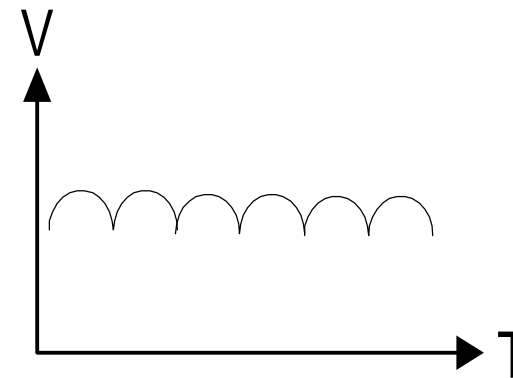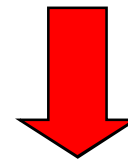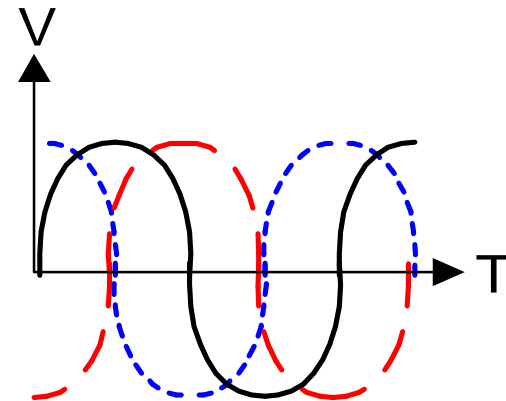Rockwell utilizes a SCR Bridge consisting of six (6) SCR/ diode sets, 2 per phase.




VFD BASIC


Diode and SCR



Turn to the Experts™

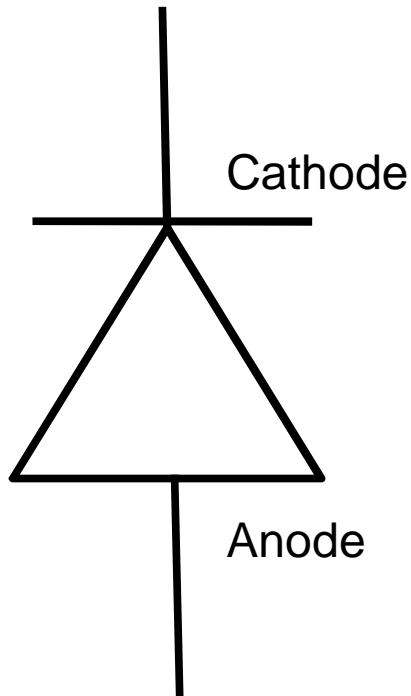

DIODE

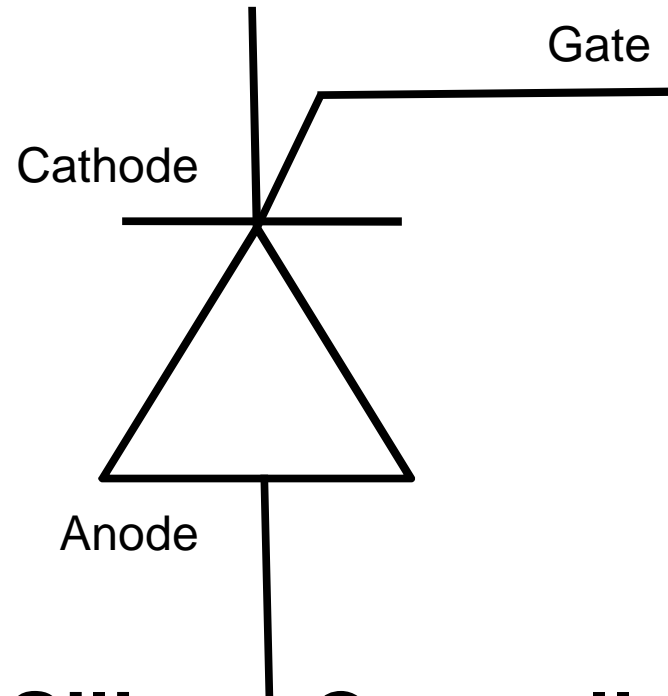


Silicon Controlled Rectifier (SCR)

VFD BASIC



Turn to the Experts™

Diode and SCR

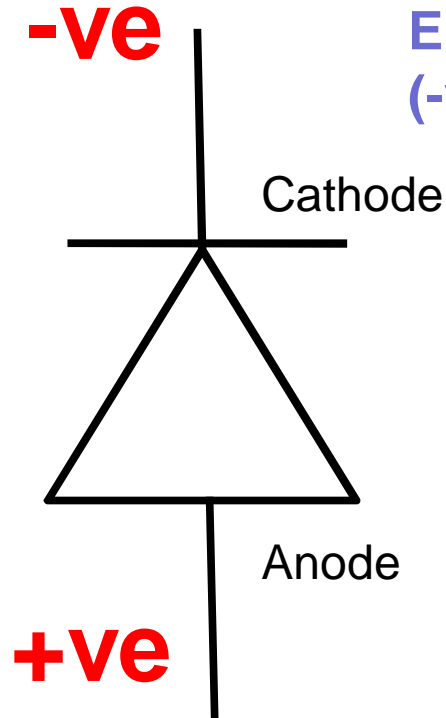

DIODE


Electron Flow
(-ve to +ve)



=



Conventional
Current flow

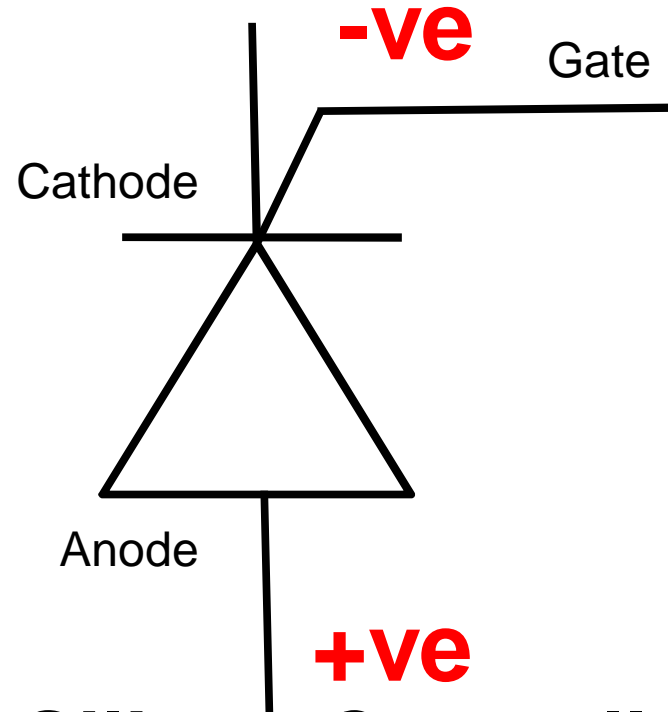


Silicon Controlled Rectifier (SCR)

VFD BASIC



Turn to the Experts™

Diode and SCR

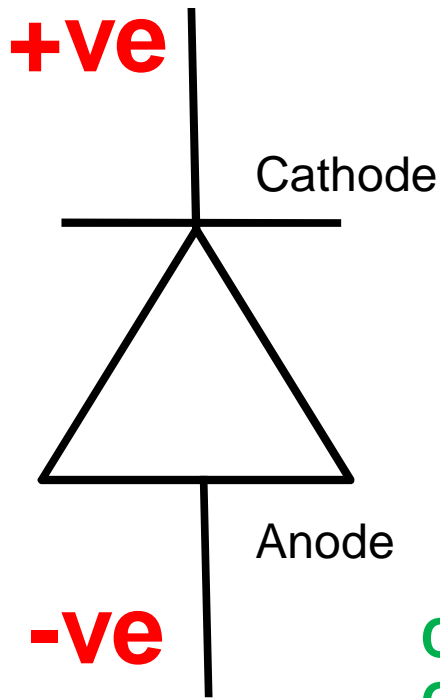


DIODE

Electron Flow
(-ve to +ve)



=

Conventional
Current

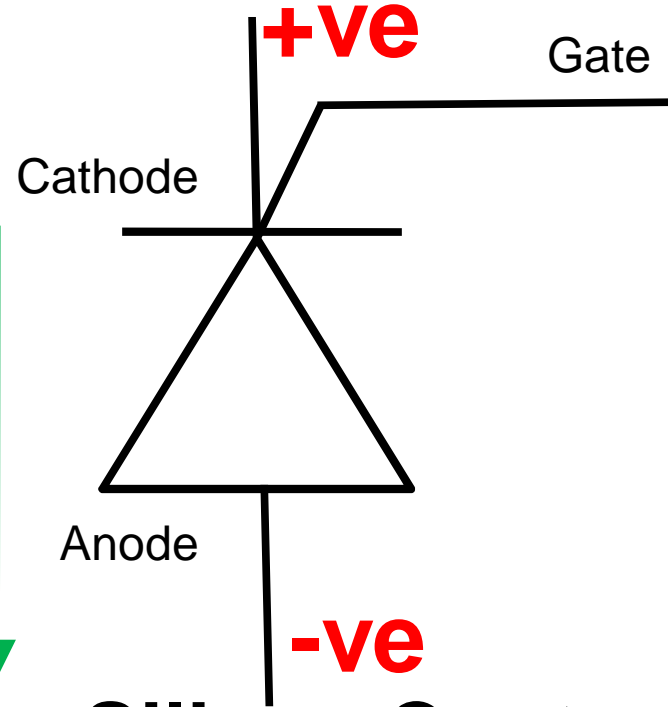

Silicon Controlled Rectifier (SCR)







VFD BASIC



Turn to the Experts™

Performing diode test

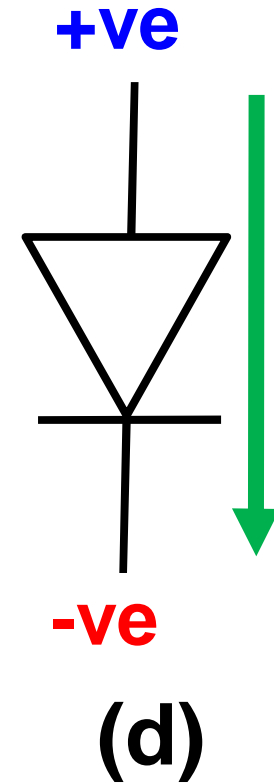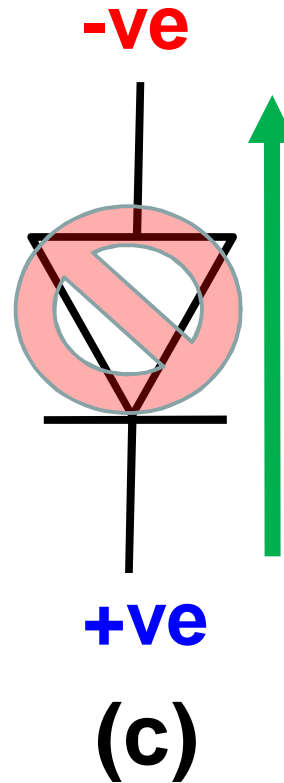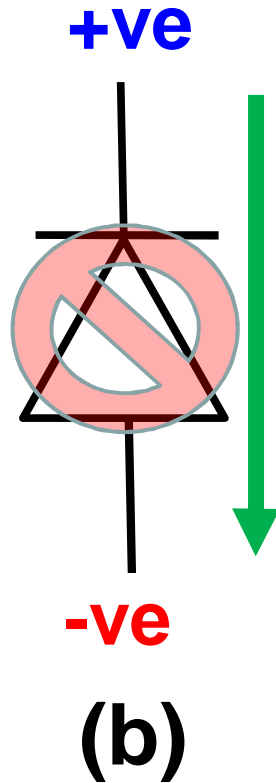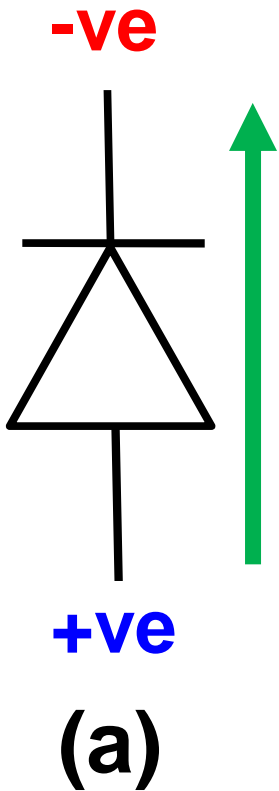


When performing diode test on VFD, **-ve** and **+ve** shown above will be the leads on your meter

VFD BASIC



Turn to the Experts™

Performing diode test

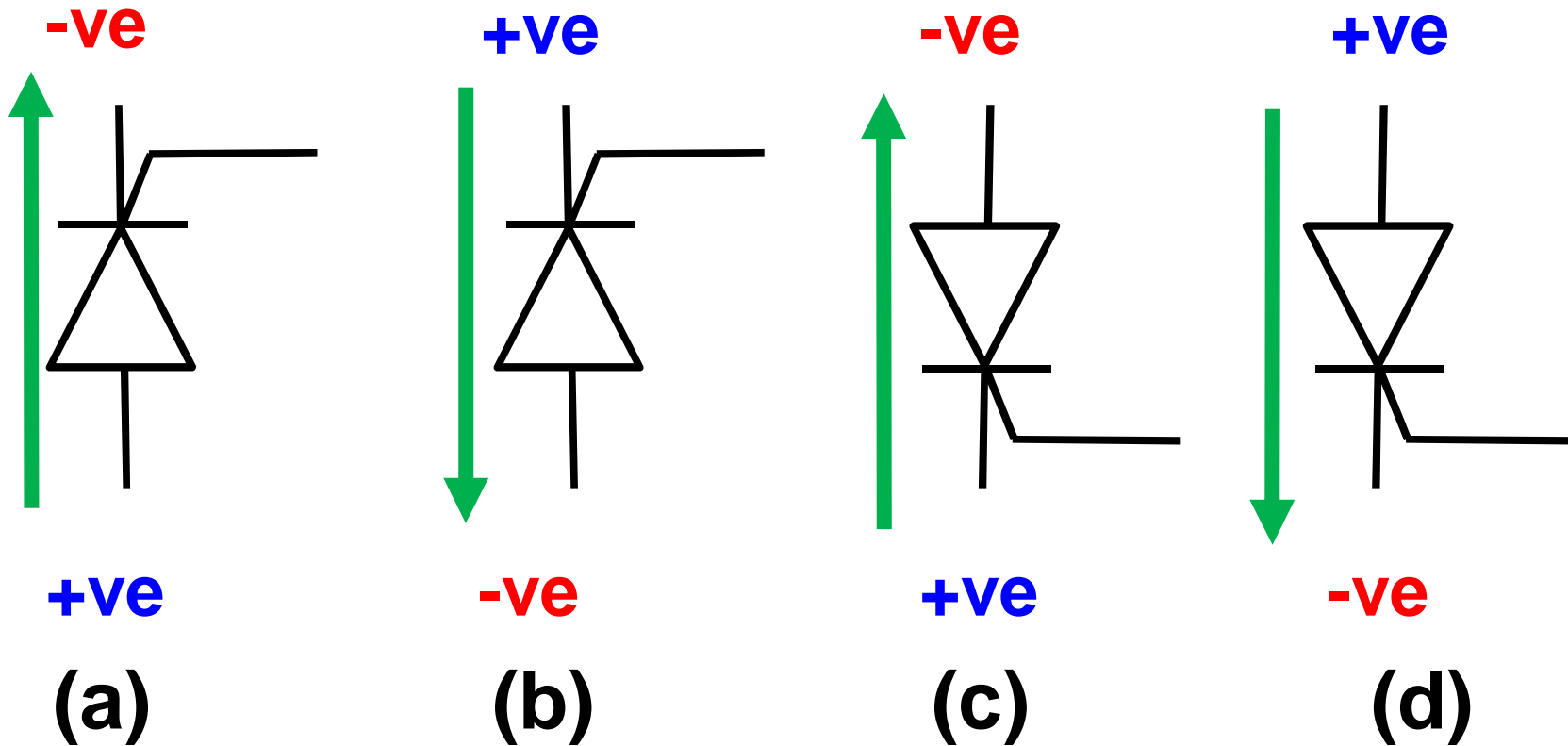


When performing diode test on VFD, **-ve** and **+ve** shown above will be the leads on your meter

VFD BASIC



Turn to the Experts™

Performing diode test

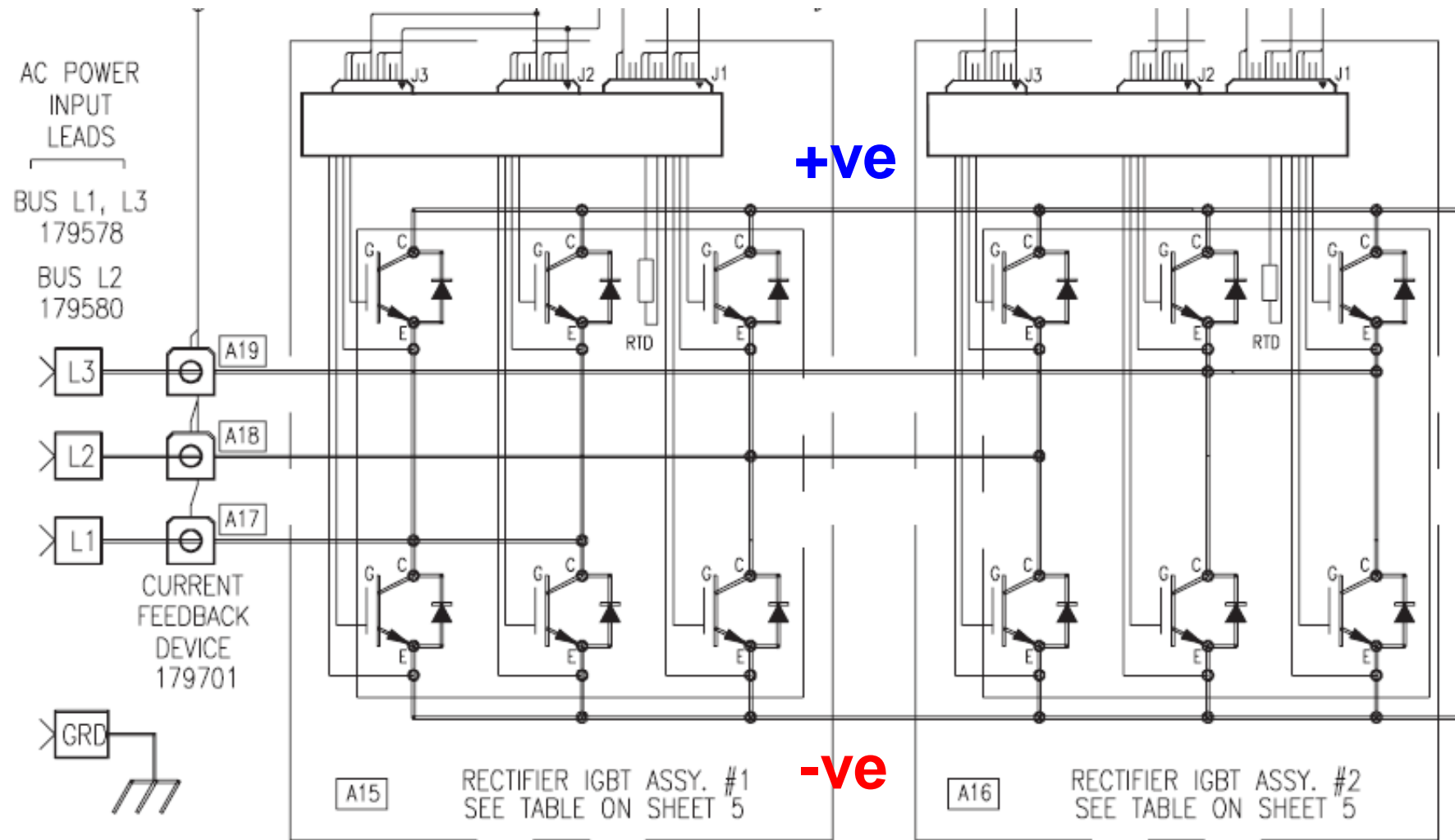


VFD BASIC

Performing diode test



Turn to the Experts™

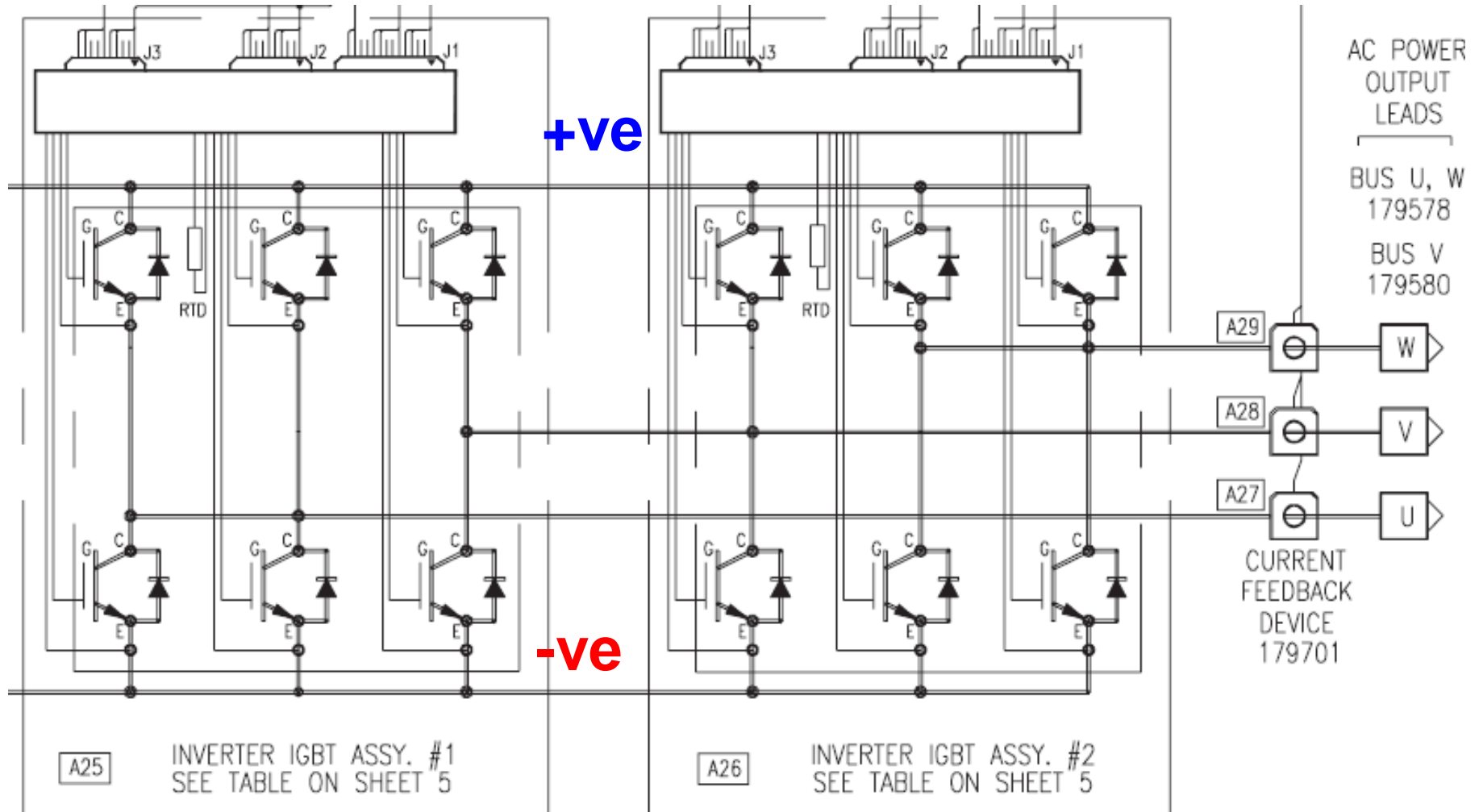

VFD BASIC



Turn to the Experts.™

Performing diode test

Table 7 — Diode Checks

METER LEAD		METER READING
(+)	(-)	
R	DC+	0.5 V
S	DC+	0.5 V
T	DC+	0.5 V
R	DC-	infinite (OL)
S	DC-	Infinite (OL)
T	DC-	Infinite (OL)
U	DC+	0.5 V
V	DC+	0.5 V
W	DC+	0.5 V
U	DC-	infinite (OL)
V	DC-	Infinite (OL)
W	DC-	Infinite (OL)
DC+	R	Infinite (OL)
DC+	S	Infinite (OL)
DC+	T	Infinite (OL)
DC-	R	0.5 V
DC-	S	0.5 V
DC-	T	0.5 V
DC+	U	Infinite (OL)
DC+	V	Infinite (OL)
DC+	W	Infinite (OL)
DC-	U	0.5 V
DC-	V	0.5 V
DC-	W	0.5 V


19/23-2SS
Page 22

VFD BASIC



Turn to the Experts™

Rectifier

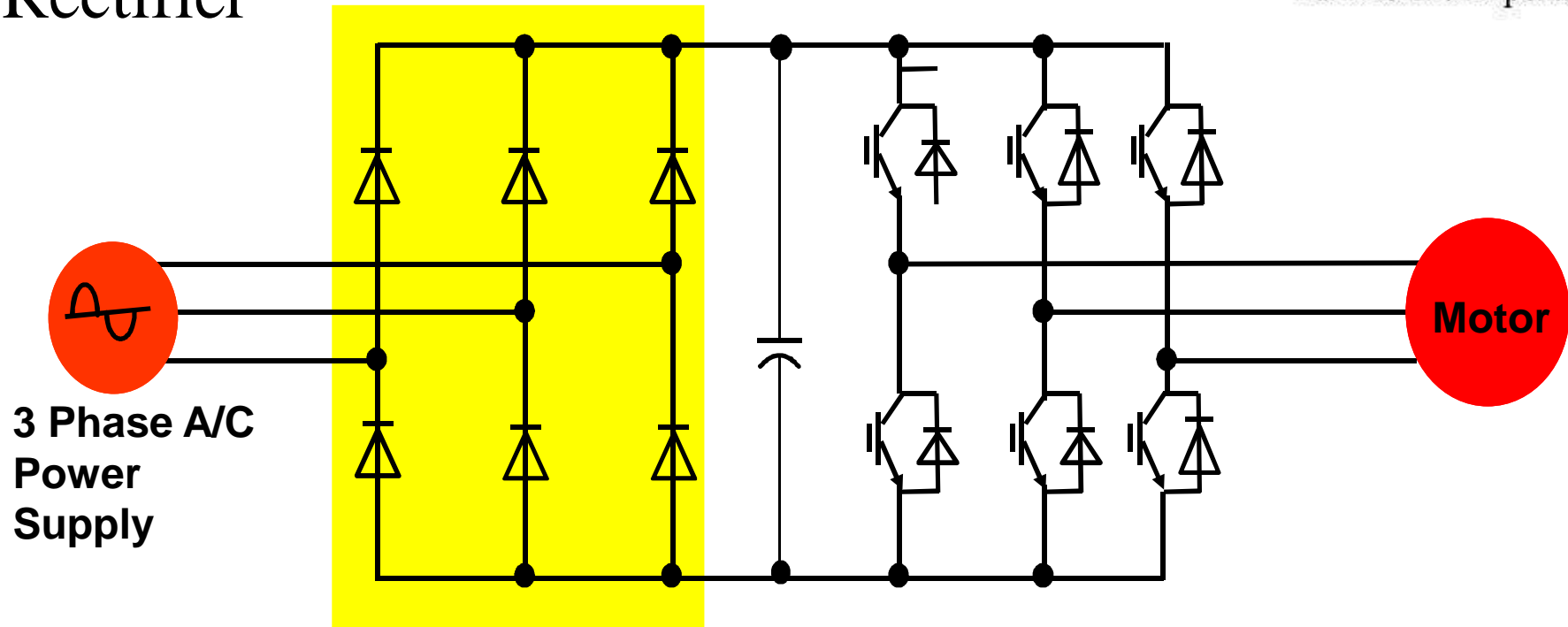

The rectifier section of the drive takes three phase a/c power and converts it to single phase d/c power

One rectifier for positive voltage, one rectifier for negative voltage, 2 rectifiers per phase

3 phase power will required minimum 6 rectifiers (6 pulses)

May contain diodes, SCR, or transistors

VFD BASIC



Turn to the Experts.™

DC Bus Capacitor

Filter (“Smooths out”) the DC Voltage ripple

Capacitor resists an abrupt change in voltage

Stores energy when a voltage appears across it

When rectifier output drops off, the capacitor will take over and furnish the load

May contain inductors, dc links, chokes etc to smooth out incoming power to DC bus

Change out power module if capacitor leaks



VFD BASIC




Turn to the Experts.™

Inverter

Change DC waveform back to AC

Create sine wave to motor using pulse width modulation (PWM)

IGBT – Insulated Gate Bipolar Transistor

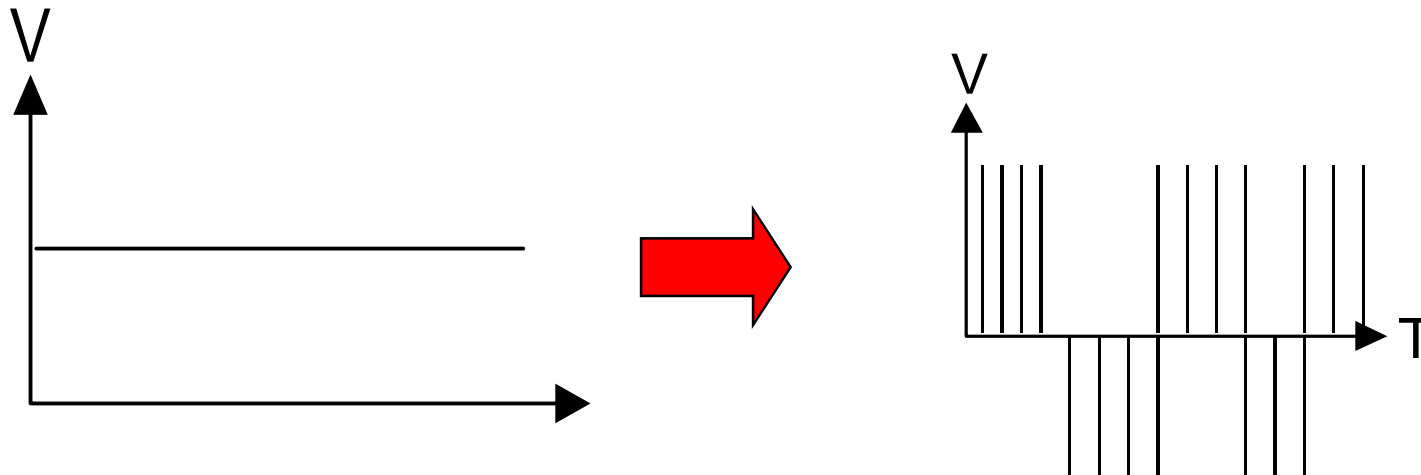

VFD BASIC




Turn to the Experts™


Transistor

A transistor is a solid-state device using the element silicon or germanium.

NPN Transistors

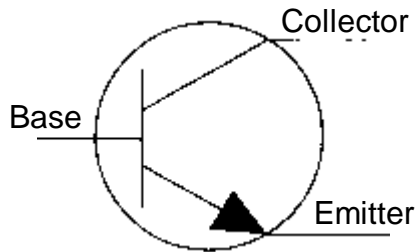


PNP Transistors

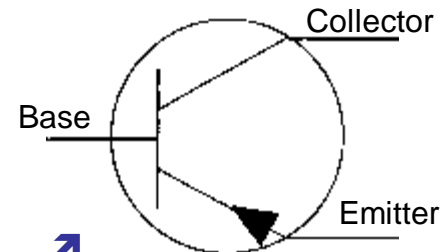


Standard Transistors

NPN IGBT

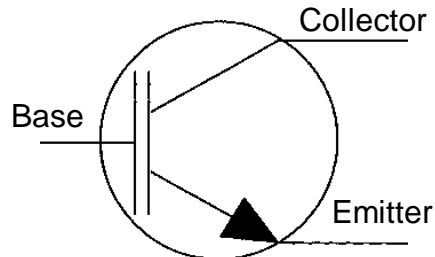

PNP IGBT

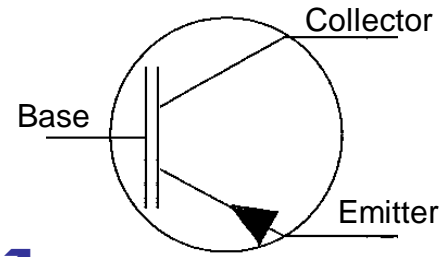

IGBT Transistors

Double line on base if IGBT transistors

Insulated gate bipolar transistor – separate base from other transistors to prevent leakage current through base of emitter/collector


IGBT insures 100% current flows through emitter & collector

VFD BASIC




Turn to the Experts™

Insulated Gate Bipolar Transistor (IGBT)

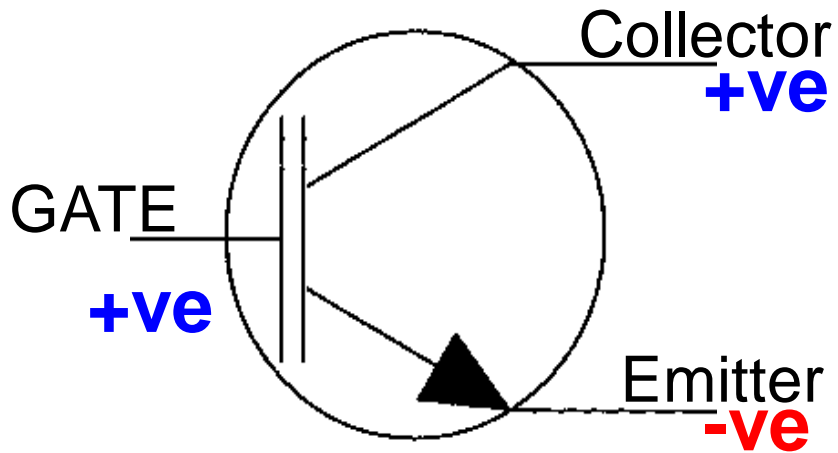

Flow

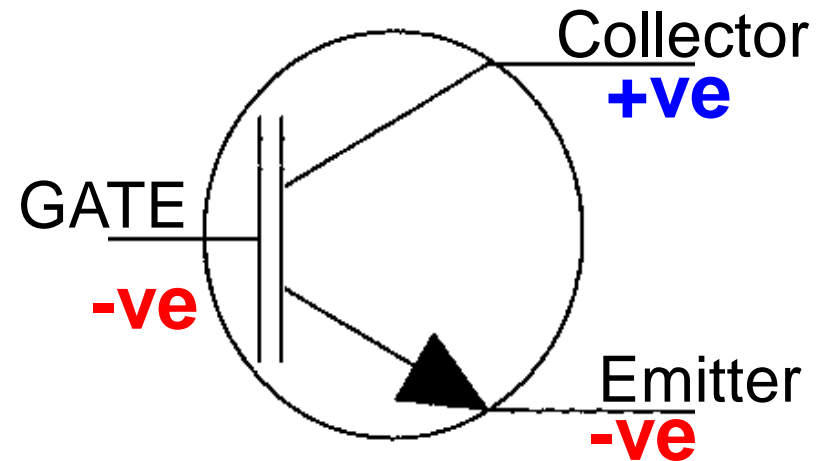


High switching capabilities

IGBT can switch on/off several thousand times per second⁵¹

VFD BASIC

Inverter

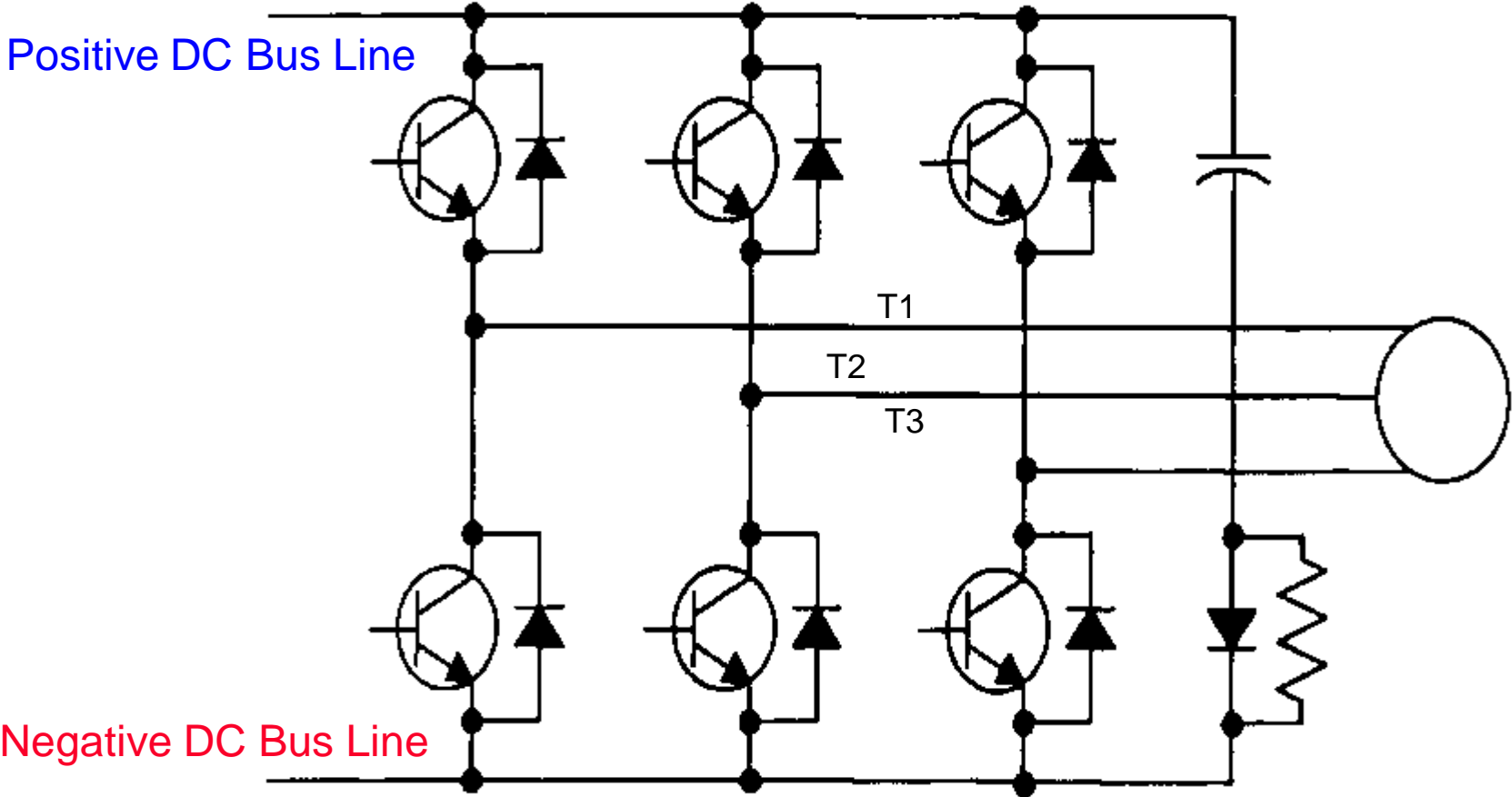


VFD BASIC



Turn to the Experts™

Transistor & Diode

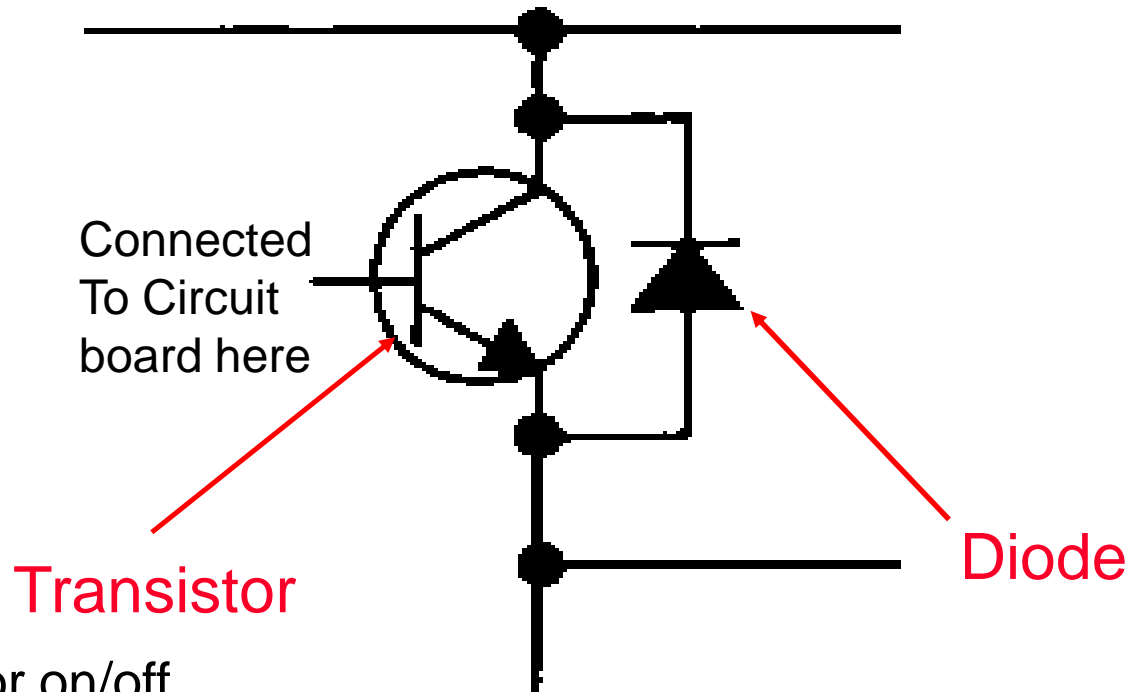

Transistor on/off

Longer ON Pulses – higher voltage

Longer OFF Pulses – lower voltage

Switching frequency – Speed pulses On/Off

2KHZ – 2000 times per second

The duration and speed of pulses combined is what is known as Pulse width modulation (PWM)


Higher frequency – smoother waveform, more heat

VFD BASIC

Electrical Basic: Kirchoff's Current Law



Turn to the Experts™

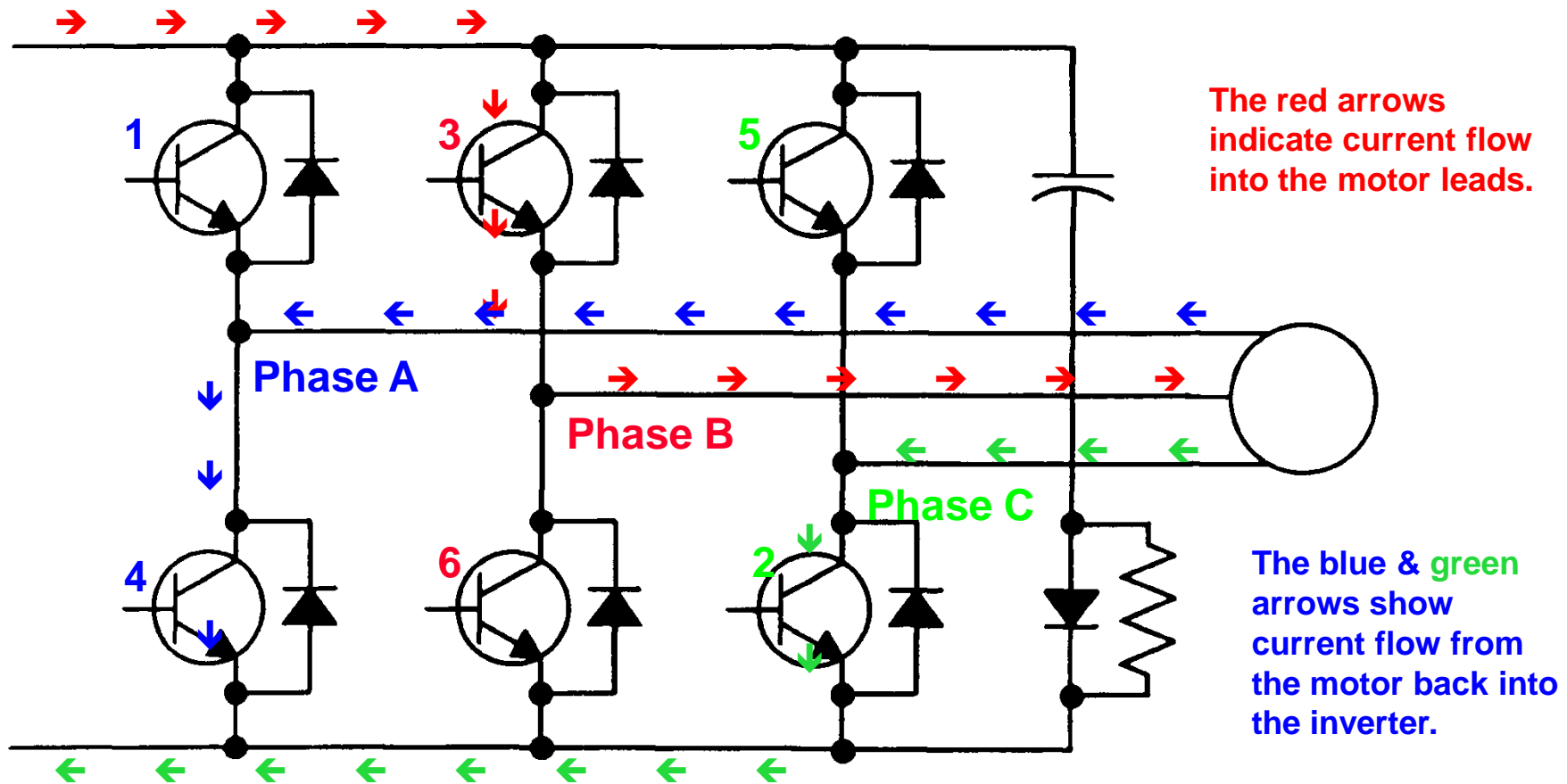

Notice that phase "A" transistor #1 is turned off & transistor #4 turned on, phase "C" transistor #2 & phase "B" transistor #3 remained on.

VFD BASIC



Turn to the Experts™

Pulse Width Modulation (PWM)

Simulated sine wave at desired frequency

$$\text{Speed} = \frac{120 \times (\text{Frequency})\text{Hz}}{\text{Number of Poles Per Phase}}$$

Electronically control a series of pulses creating a signal that closely resembles a sine wave

Drive controls when IGBT is switched on/off, and how long it is held on (width)


Wide pulses=high voltage, narrow pulse=low voltage

VFD BASIC


VFD -- Rockwell Drives



Turn to the Experts™

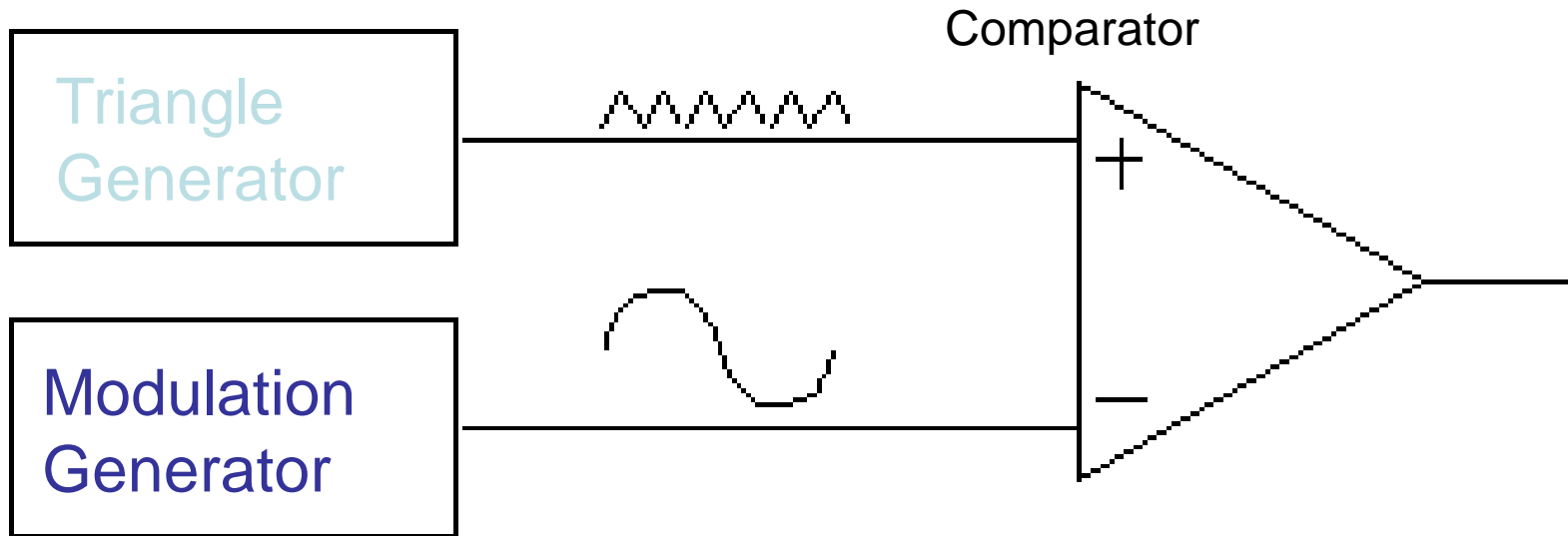

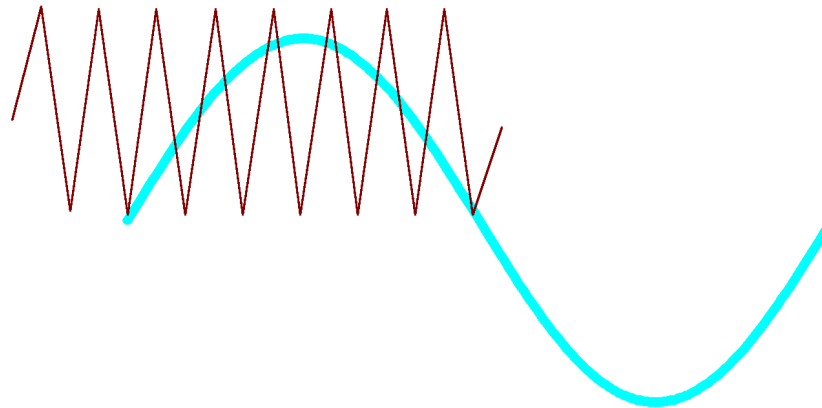Combination of
Triangular signal and
sine wave




VFD BASIC

VFD -- Rockwell Drives



Turn to the Experts™

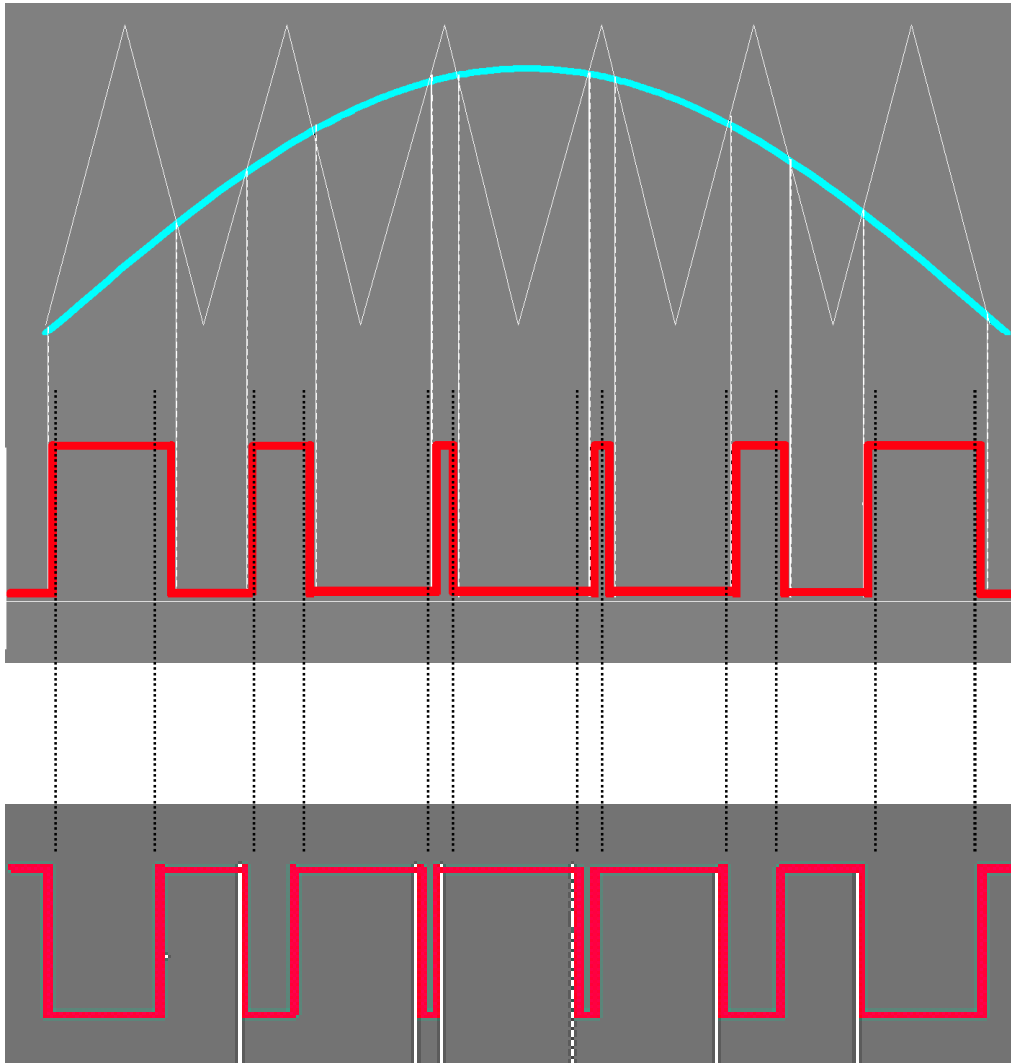


Different widths are formed based on the weighing of sine wave

VFD BASIC

VFD -- Rockwell Drives




Turn to the Experts™

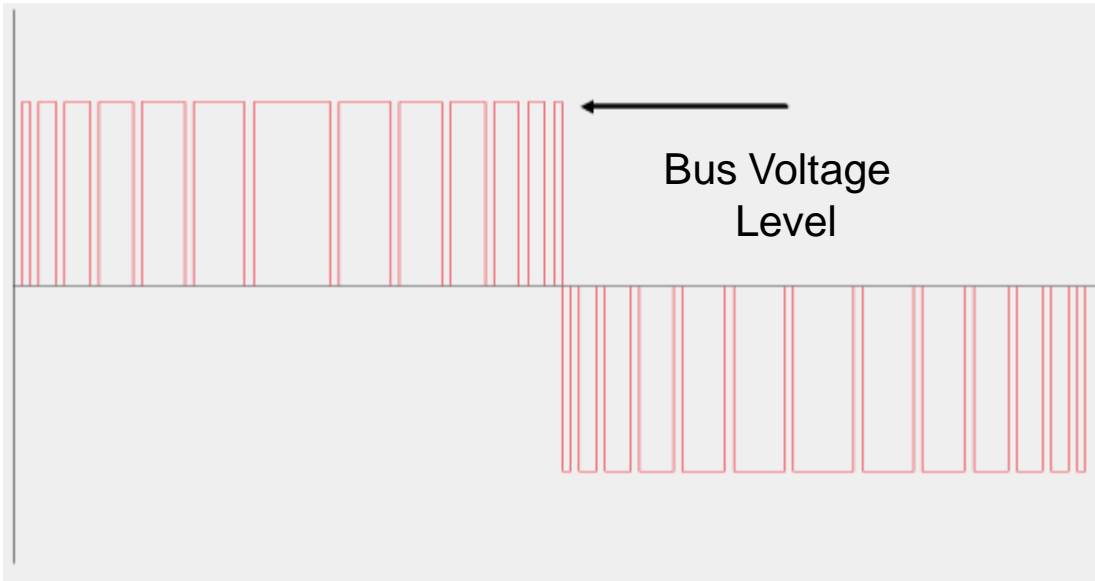

Varying pulse width will vary RMS voltage to motor

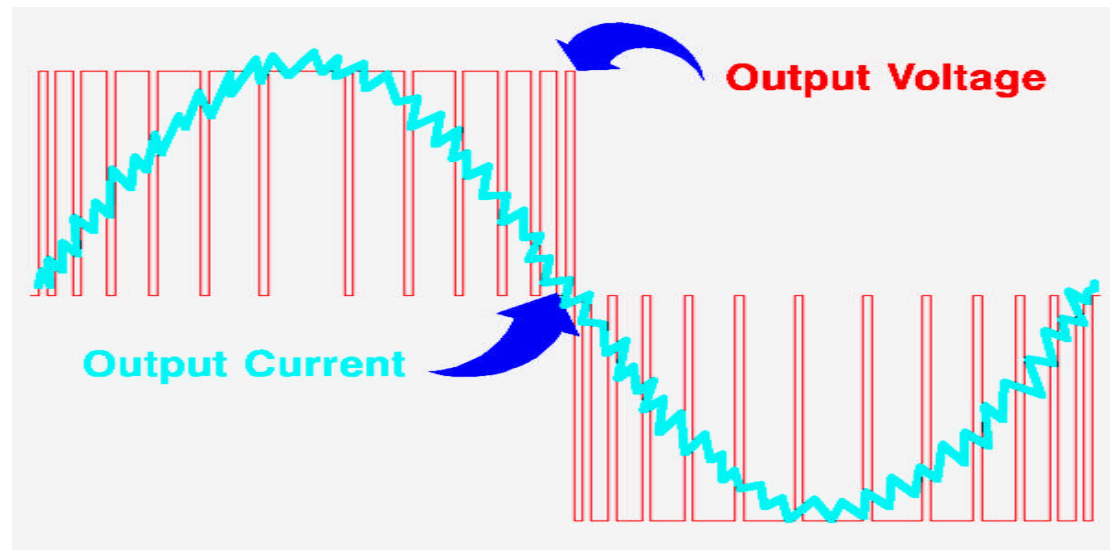Combination of Triangular signal and sine wave




VFD BASIC

VFD -- Rockwell Drives





Turn to the Experts™

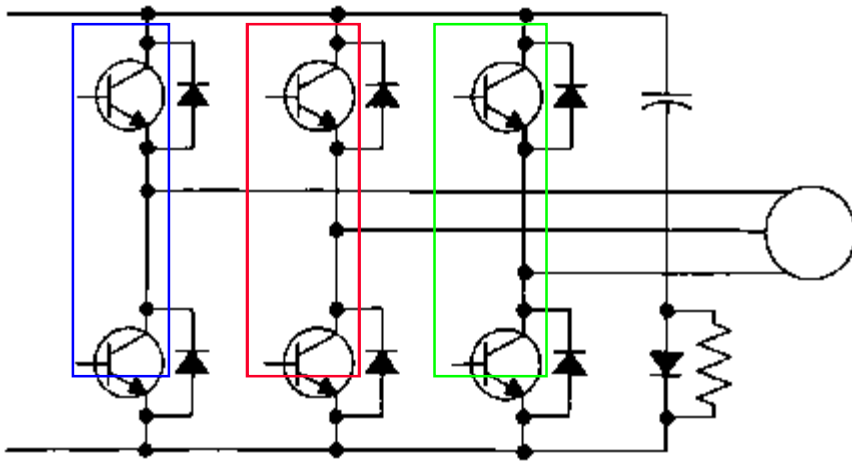

The six transistors are turned on and off in a certain order to form three phase pulse width modulated waveforms.

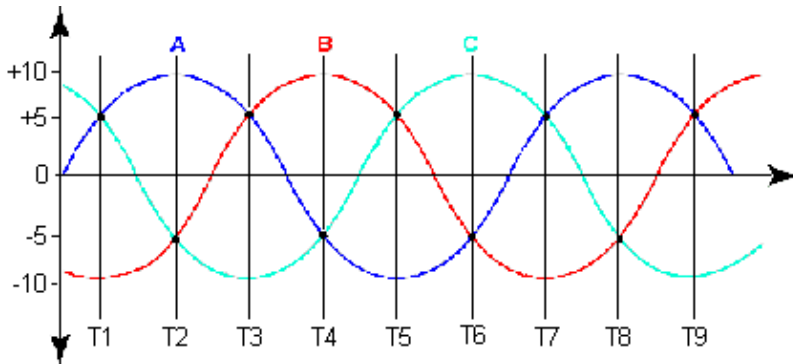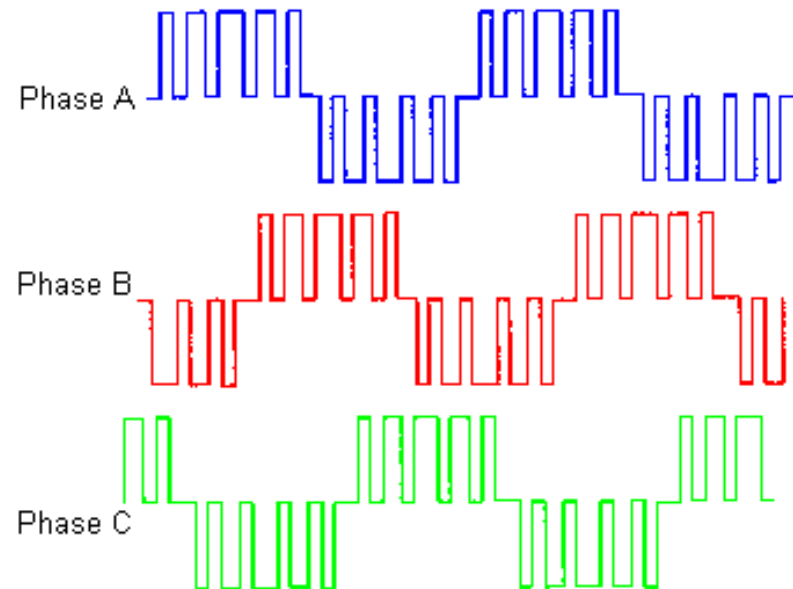The PWM waveform actually is a Square wave DC voltage. This voltage is applied directly to the AC motor terminals.



Although DC voltage is applied to the motor, the current waveform resembles an AC sine wave and is used to control speed of the AC squirrel cage induction 59 motor.

VFD BASIC

VFD -- Rockwell Drives






Turn to the Experts™

Example:

Phase A

Transistor 1 turn on/off on positive 1/2 cycle; Transistor 4 turn on/off on negative 1/2 cycle

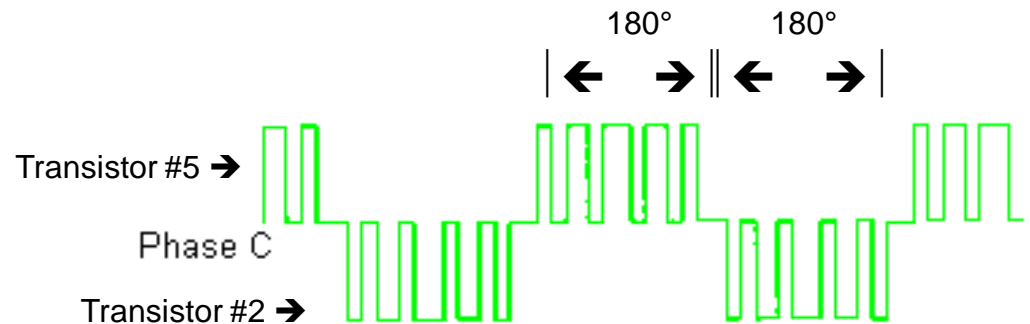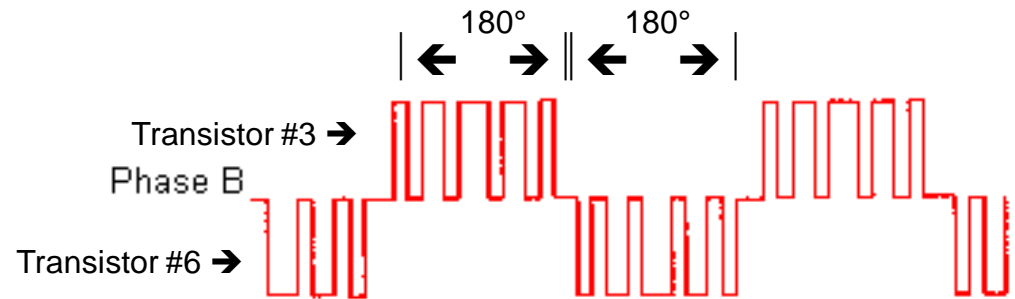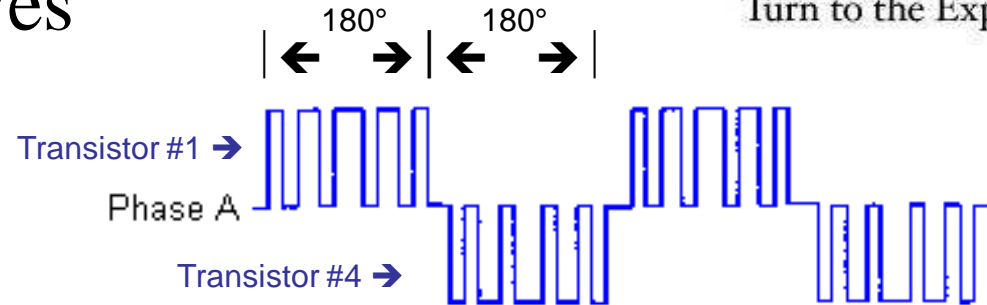This is the same for Phase B and Phase C except with phase shift




Note: the positive half cycle for B starts 120 degrees after the positive half cycle for A phase, C starts 240 degrees after A.

VFD BASIC

Power Factor



Turn to the Experts™

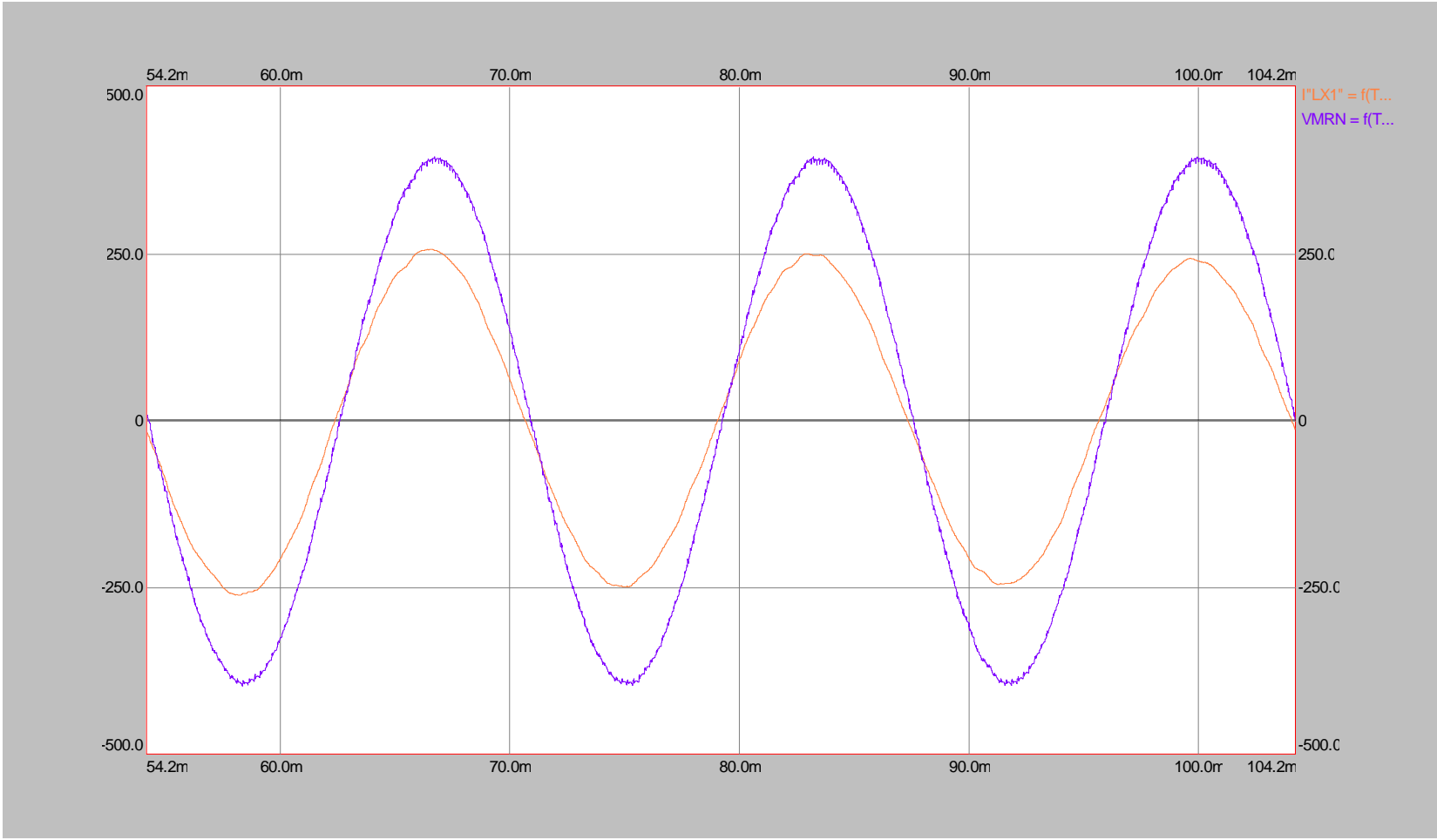

A voltage and Current Sine Wave that are in unity

VFD BASIC



Turn to the Experts™

VFD Line and Load Power Measurements at 100% load

$$\frac{\text{Line KW} = 706.7 \text{amps} \times 480 \text{vac} \times 1.73 \times 0.95 \text{ (PF)}}{1000} = 557 \text{KW}$$


$$\frac{\text{Load KW} = 823.2 \text{amps} \times 447 \text{vac} \times 1.73 \times 0.843}{1000} = 536 \text{KW}$$

$$\frac{\text{Load KW (536KW)}}{\text{Line KW (557KW)}} = 0.962$$

This identifies a drive loss of approximately 3.5% that occurs in a VFD operating at 100% load


VFD BASIC

Drive Design -- Rectifier

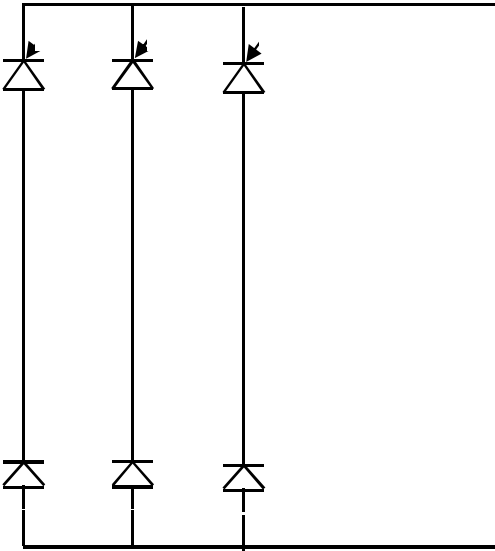

Combination of Diodes

Passive Design

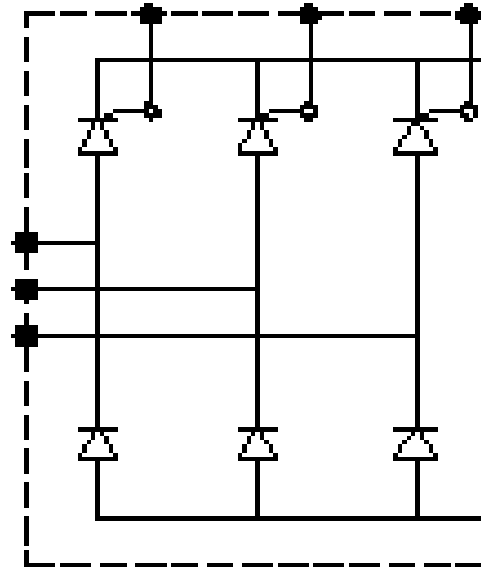


Combination of SCR's and Diodes

Active Design



Turn to the Experts™

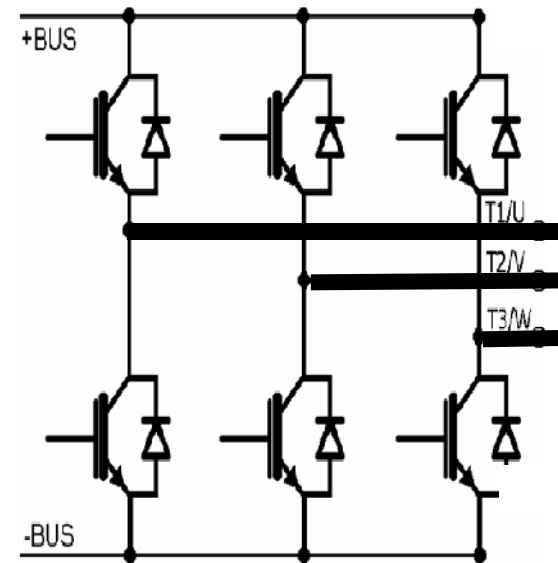


IGBT's which is referred to as an active front end or controlled

VFD BASIC

Drive Design – DC Chokes & Reactor



Turn to the Experts™

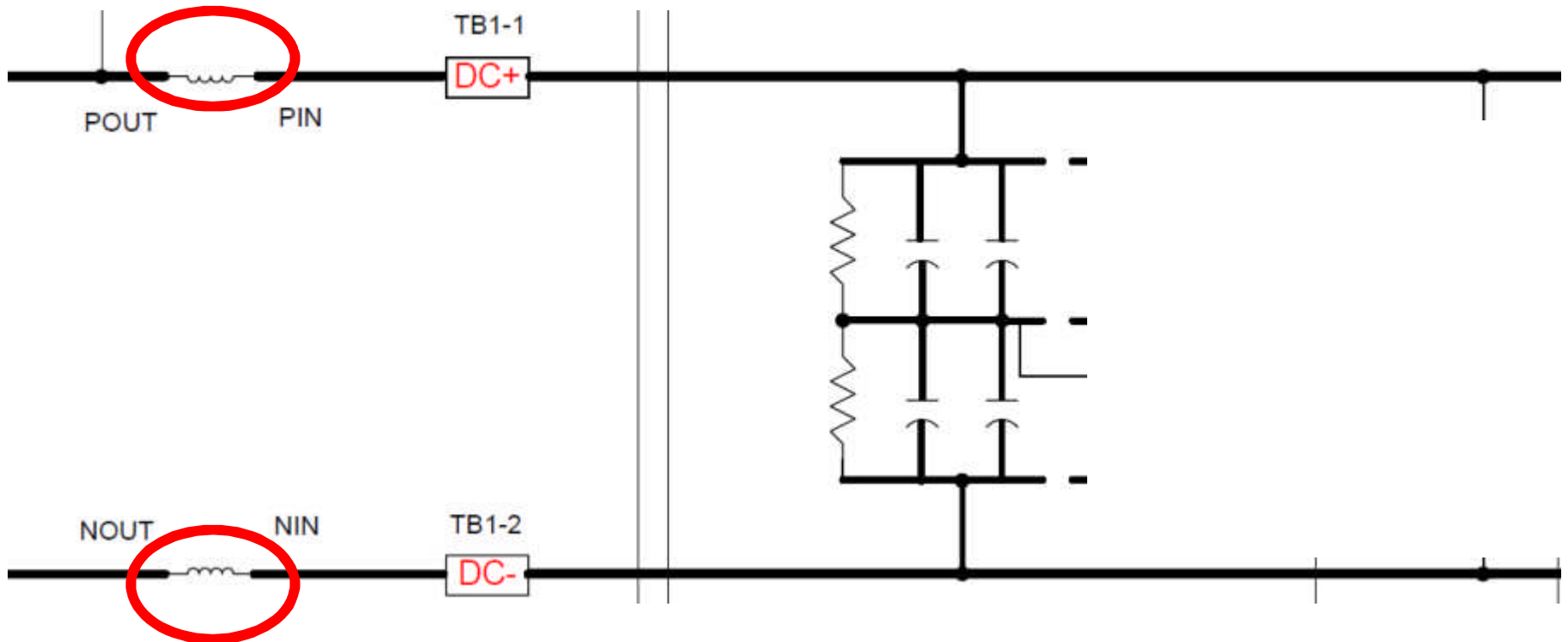

Smooth incoming power to DC bus

VFD BASIC


Drive Design – Filter Section



Turn to the Experts™

Filter Section (+)

Capacitors
installed in
series

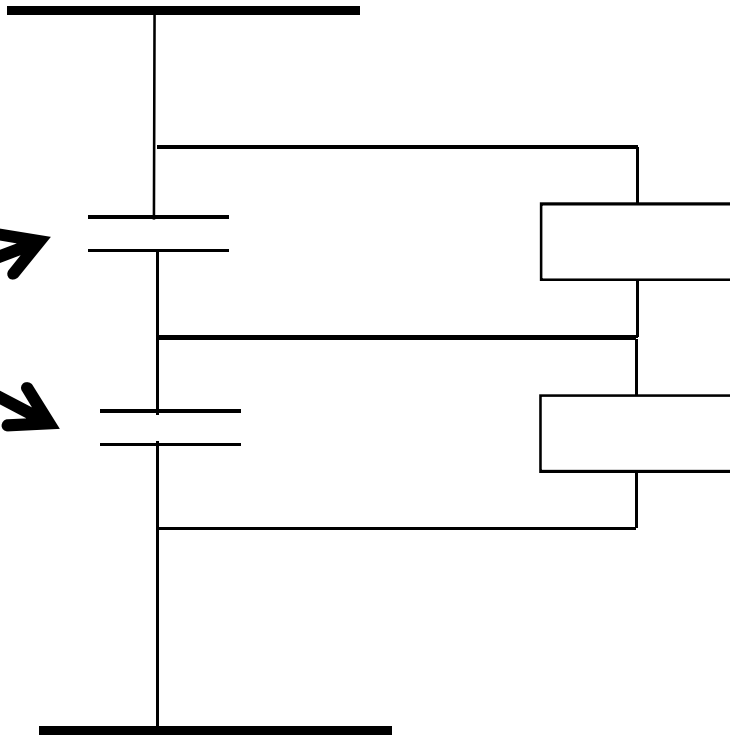


Balancing
Resistors

VFD BASIC

Drive Design -- Inverter



Turn to the Experts™

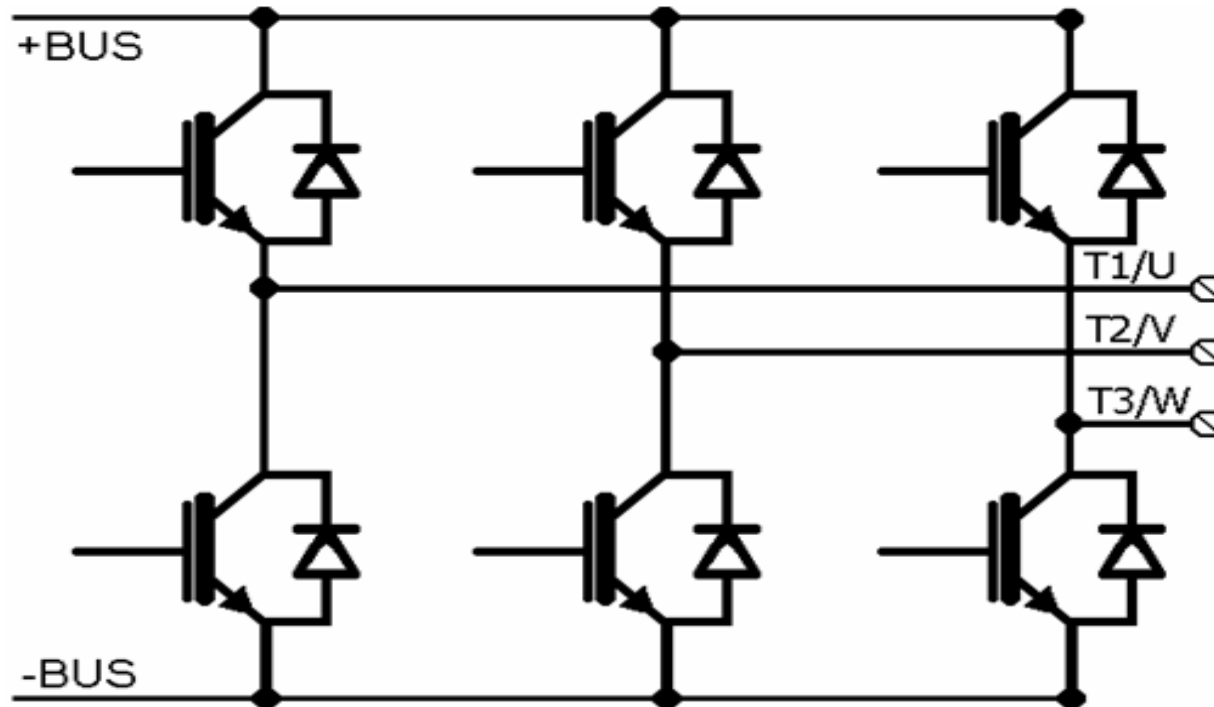

Motor


The PWM or pulse width modulated signal is set for 2Khz on the standard tier drives and either 2 or 4Khz on the Rockwell LF2 drive

VFD BASIC

Drive Design – Overload Control



Turn to the Experts.™

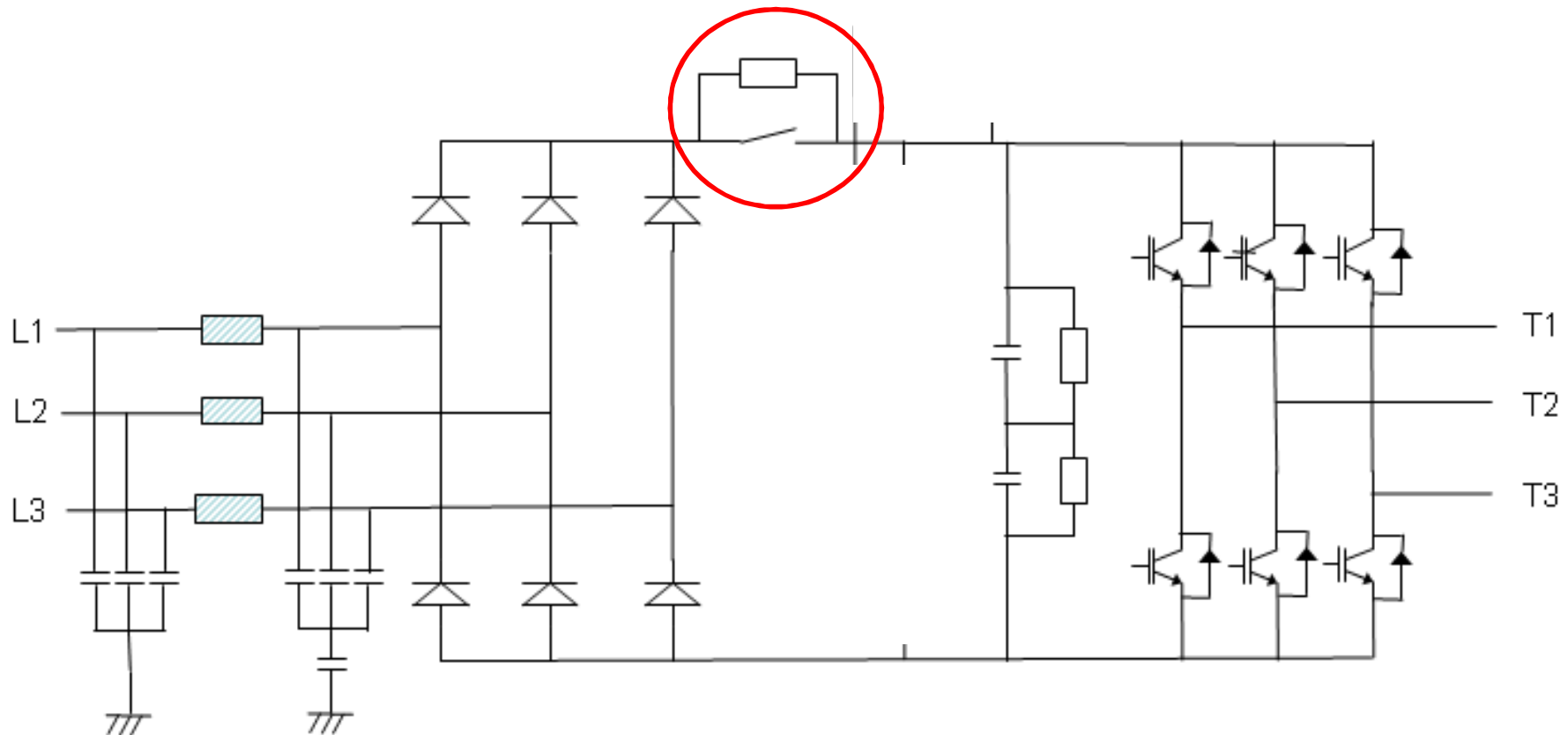

A design using a diode rectifier typically uses a resistor for the initial charging of the filter section with a bypass contactor that is engaged to bypass the resistor when the D/C bus reaches a specific voltage level


VFD BASIC



Turn to the Experts™


What do VFDs control ?

Frequency

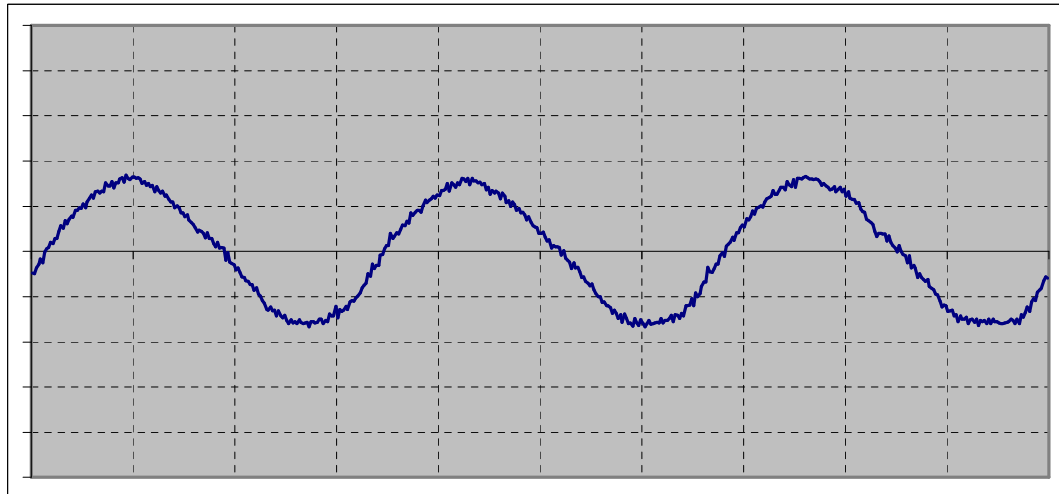

and

Voltage

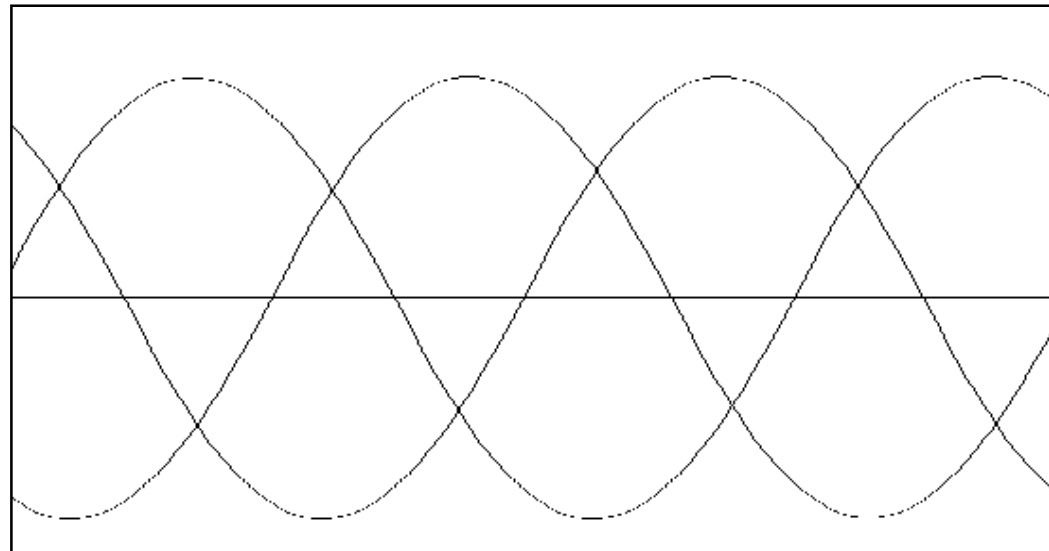

VFD BASIC



Turn to the Experts™

VFD Control Method

Sensorless Vector

VFD output control based on characteristics of motor

Necessary to have correct motor design data (voltage, current, RPM)

Better speed regulation by looking at both voltage and current

Better torque control at low speed

LF2, PF755, Eaton LCX9000 drives

Volts per Hertz

$460\text{V}/60\text{Hz} = 7.67\text{V}/\text{hz}$

Voltage changed proportionately with frequency

Drive maintain constant v/hz ratio

Unable to maintain torque at low speed


LF1 Drive

VFD BASIC



Turn to the Experts™


Volts per hertz Control Method

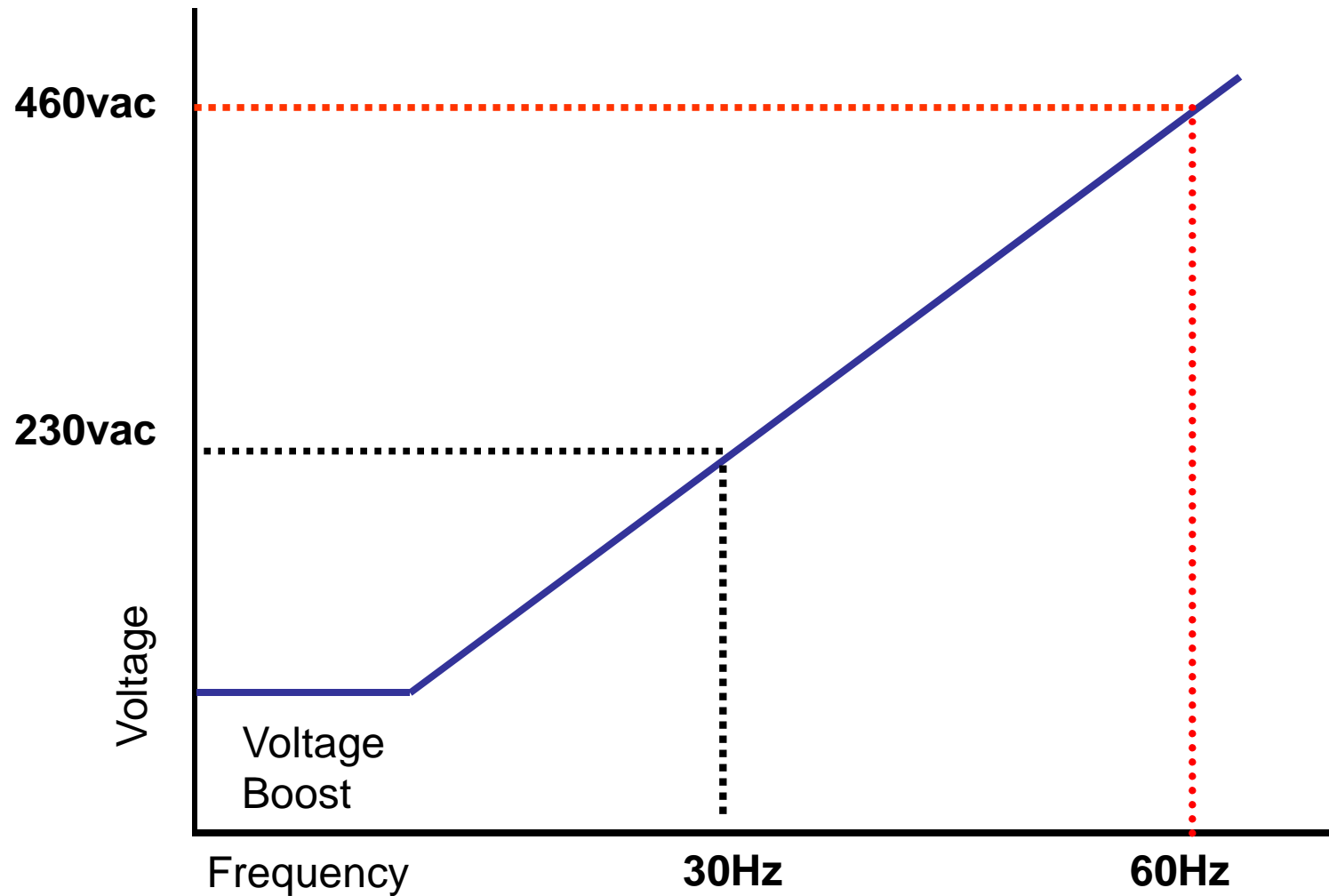

Constant volts per hertz control of the IGBTs

VFD BASIC

Drive Design

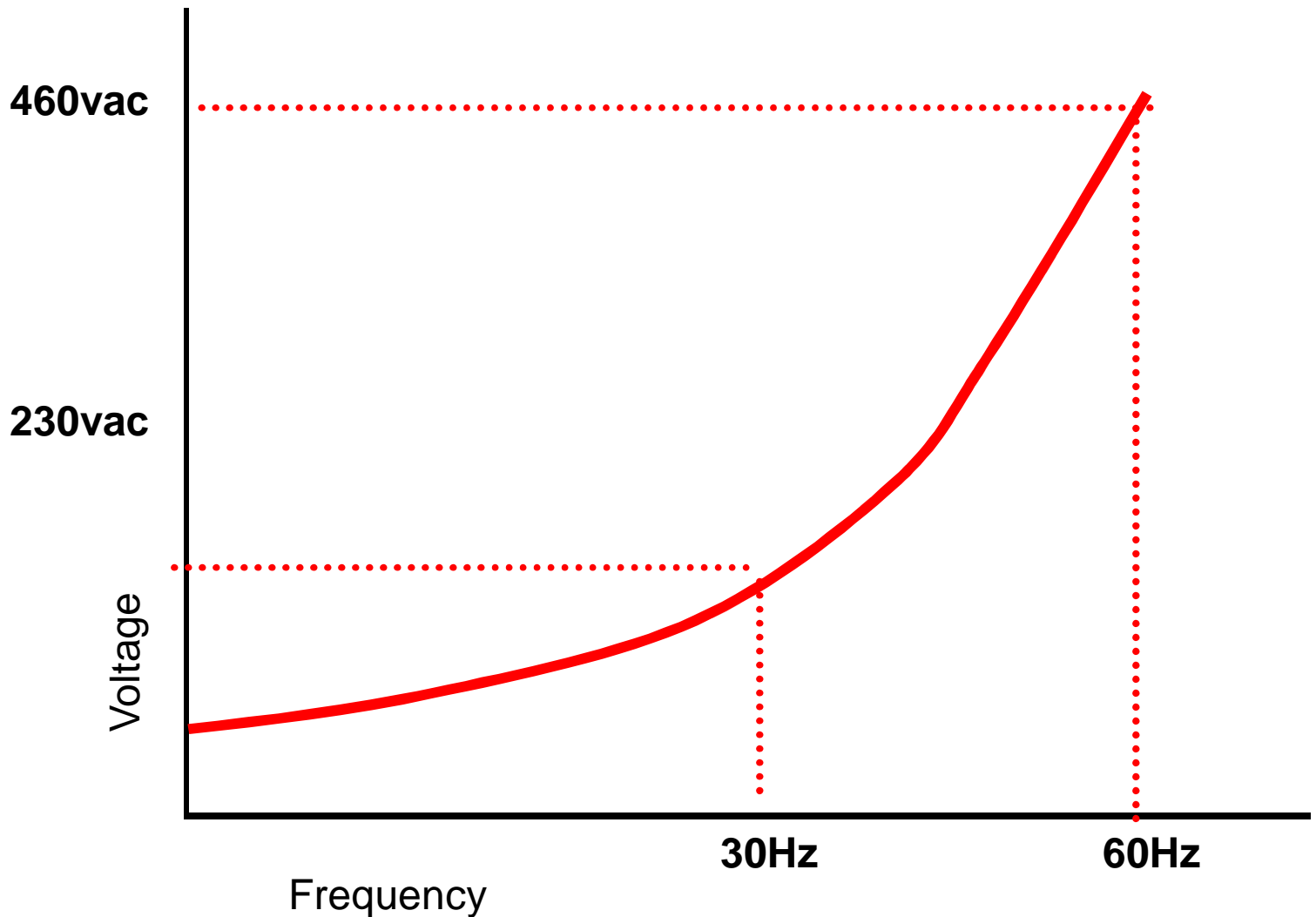

Sensorless Vector Control of the IGBTs

VFD BASIC

Harmonic Distortion



Turn to the Experts™

VFD design will affect harmonics produced

DC link inductors, drive with active front end (transistors in rectifier) have lower harmonic levels

Devices to reduce harmonics –


- Line reactors
- Passive filters (inductors, reactors and capacitors)
- Active filters
- Active front end (IGBT rectifiers)
- Higher pulse rectifier (12, 18, 24, 30 pulses)

VFD BASIC


Harmonic Distortion



Turn to the Experts™

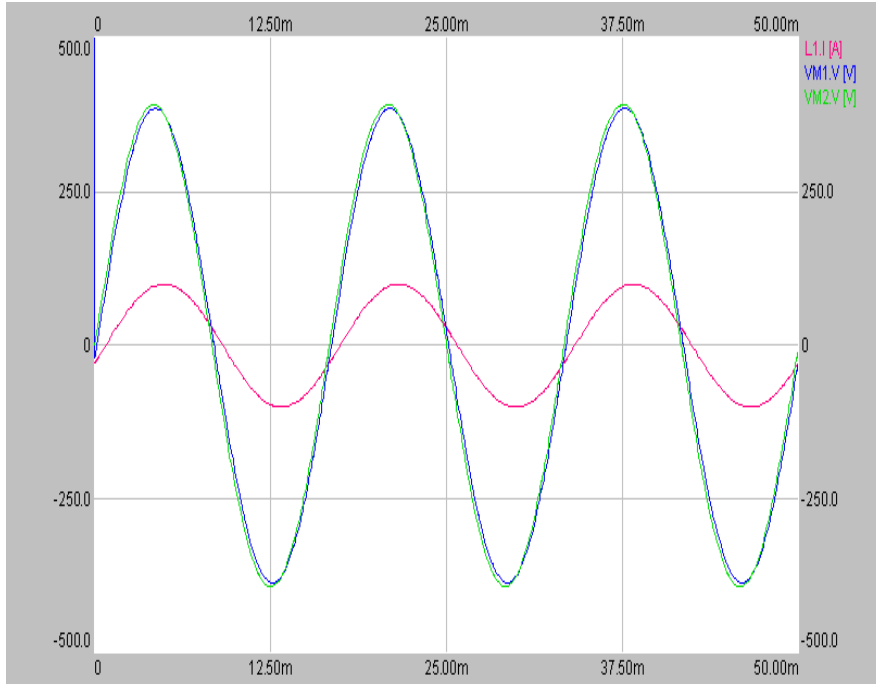

Normal Sine Wave with no distortion

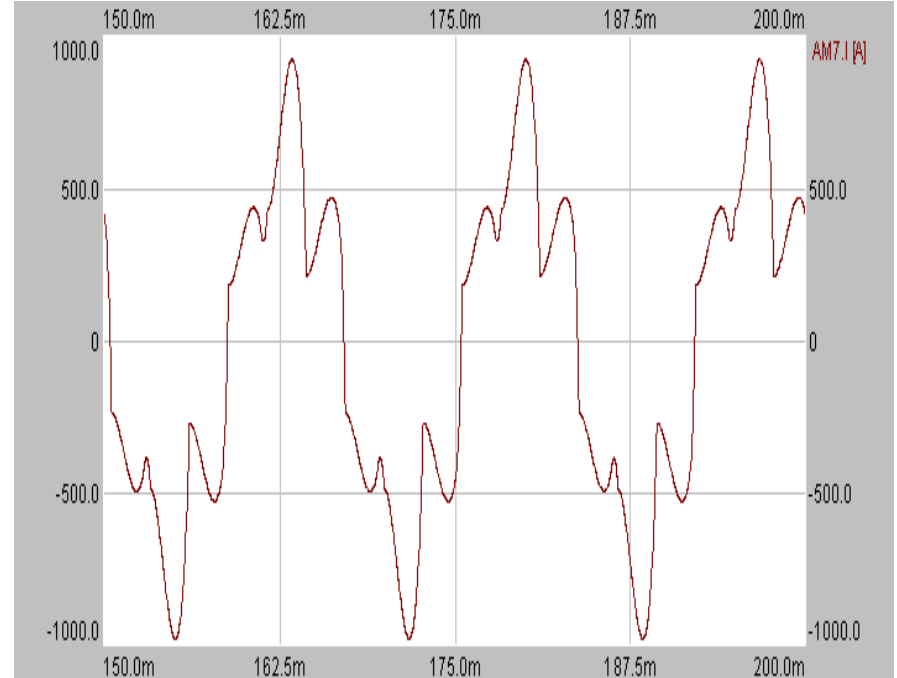


A Sine Wave with significant distortion

VFD BASIC

Harmonic Distortion



Turn to the Experts.™

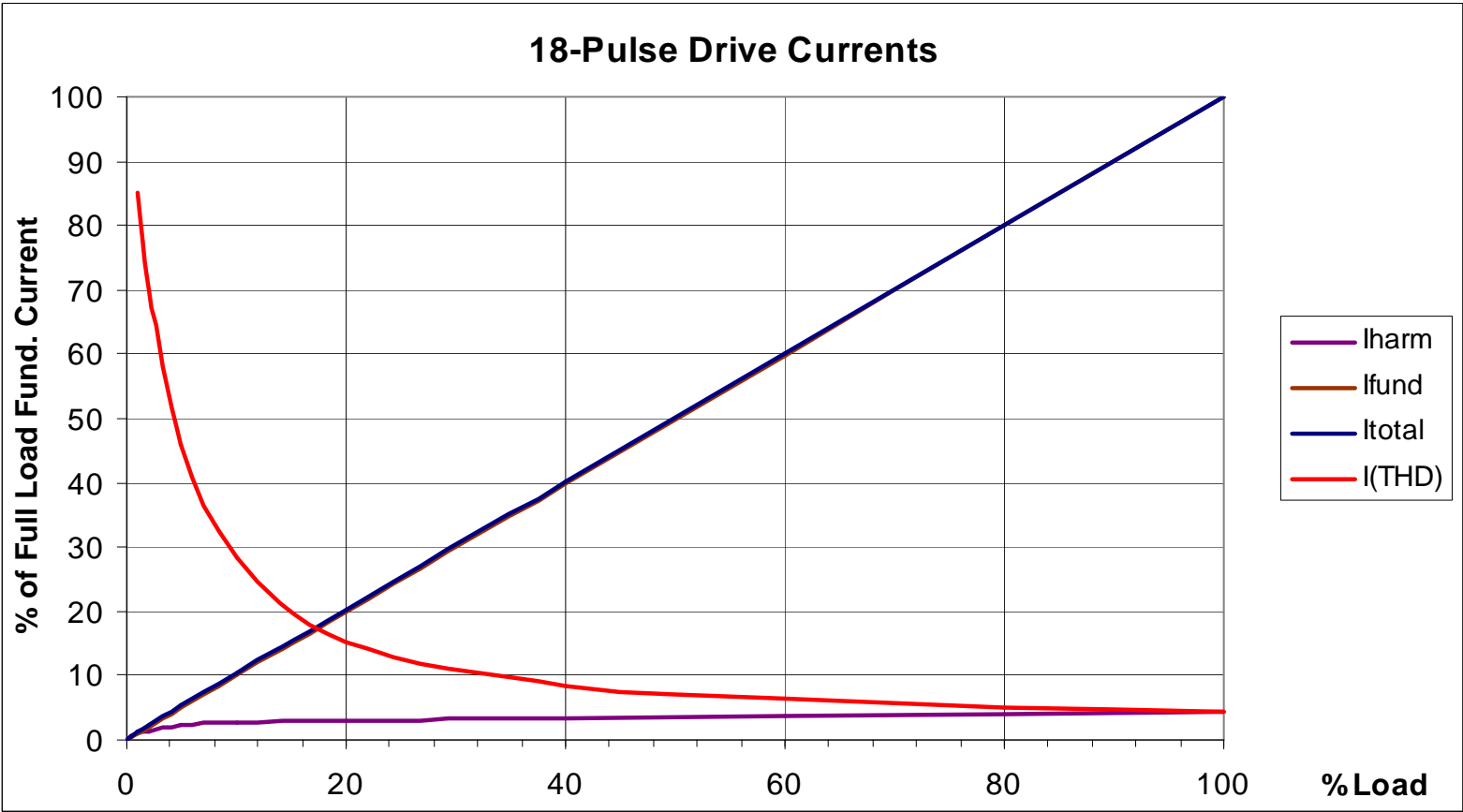


VFD BASIC


Harmonic and Line Reactors




Turn to the Experts™

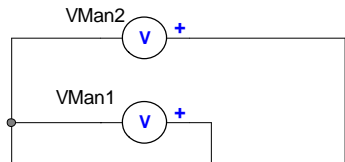

75hp, 480V Converter

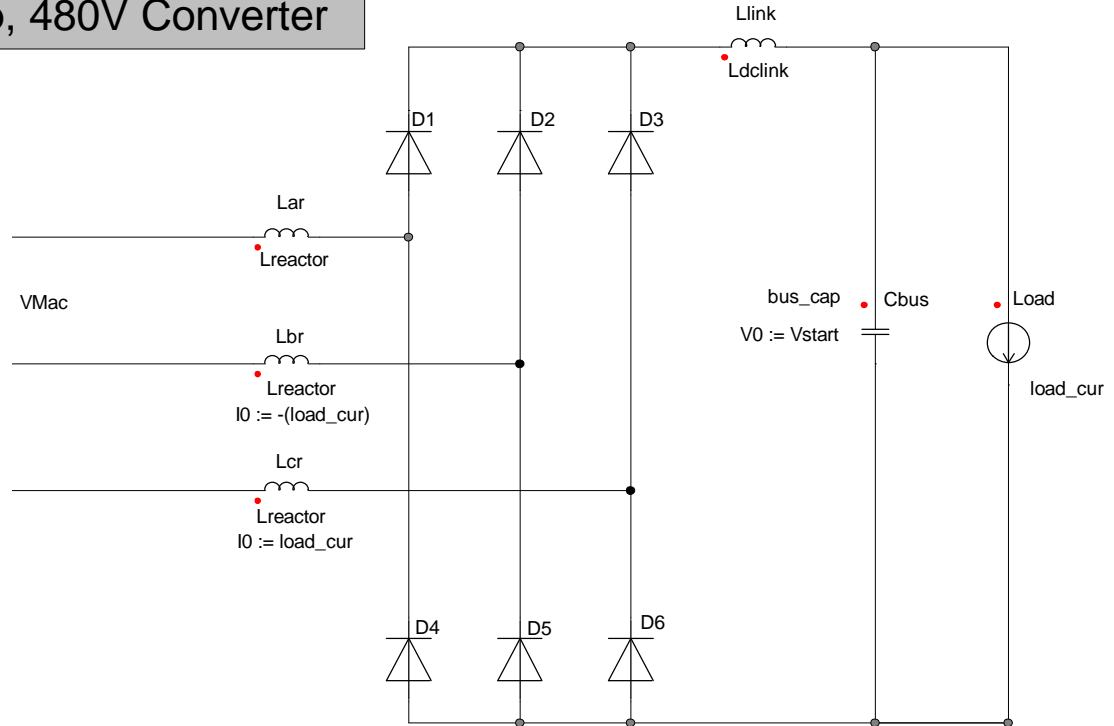

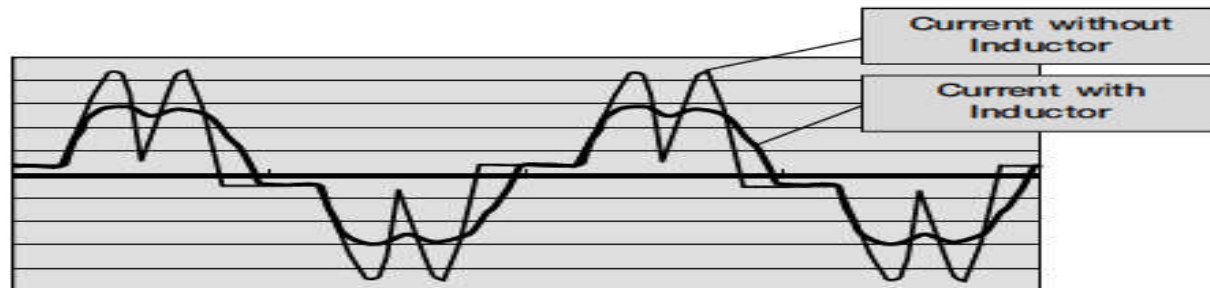Line reactors are typically offered in 3% or 5% impedance values





VFD BASIC

Passive harmonic Filters



Turn to the Experts™

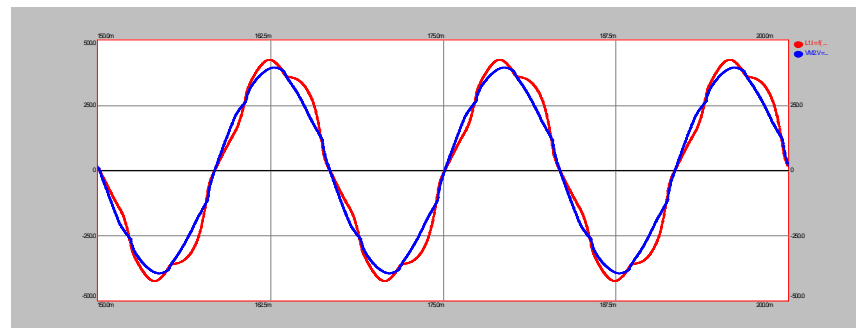
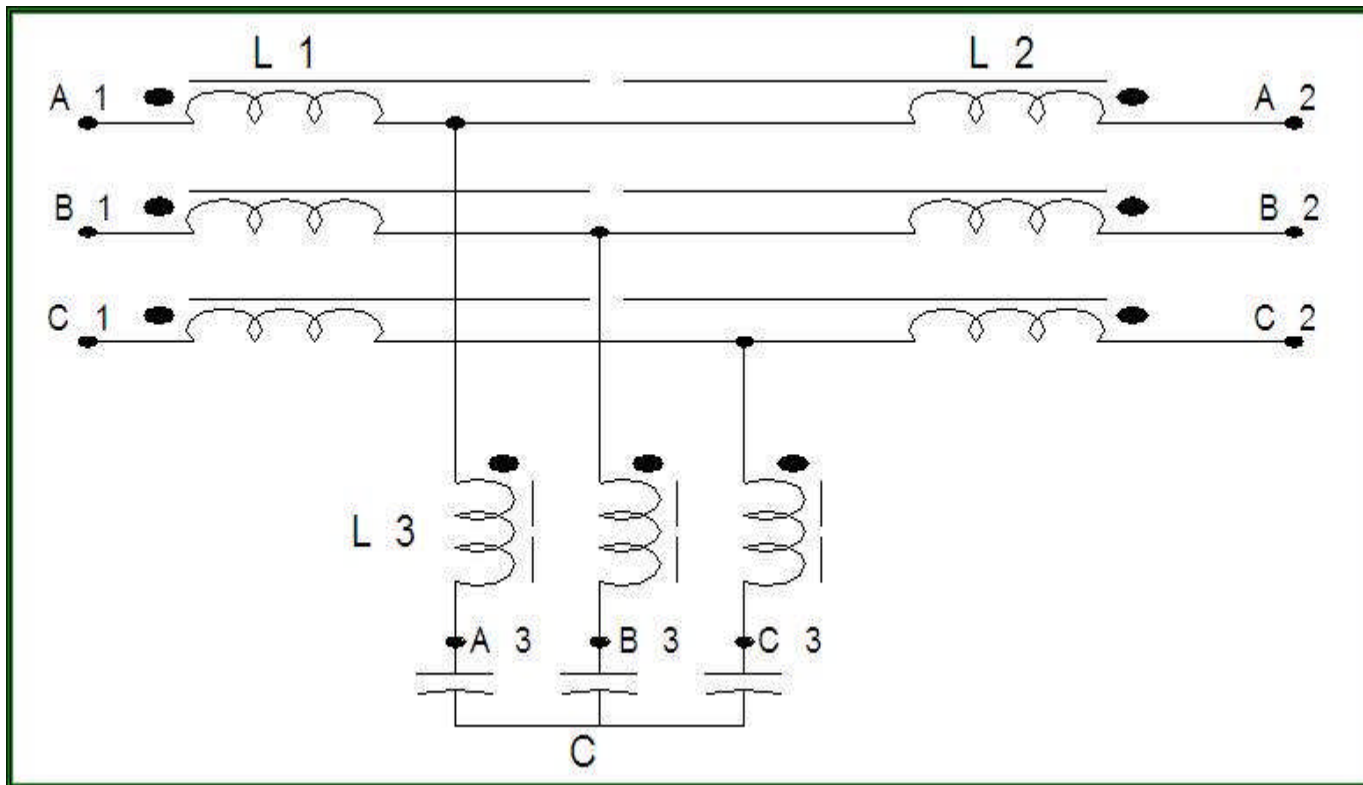


VFD BASIC

Active harmonic Filters




Turn to the Experts™

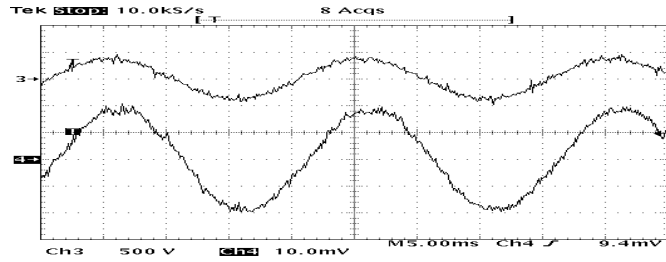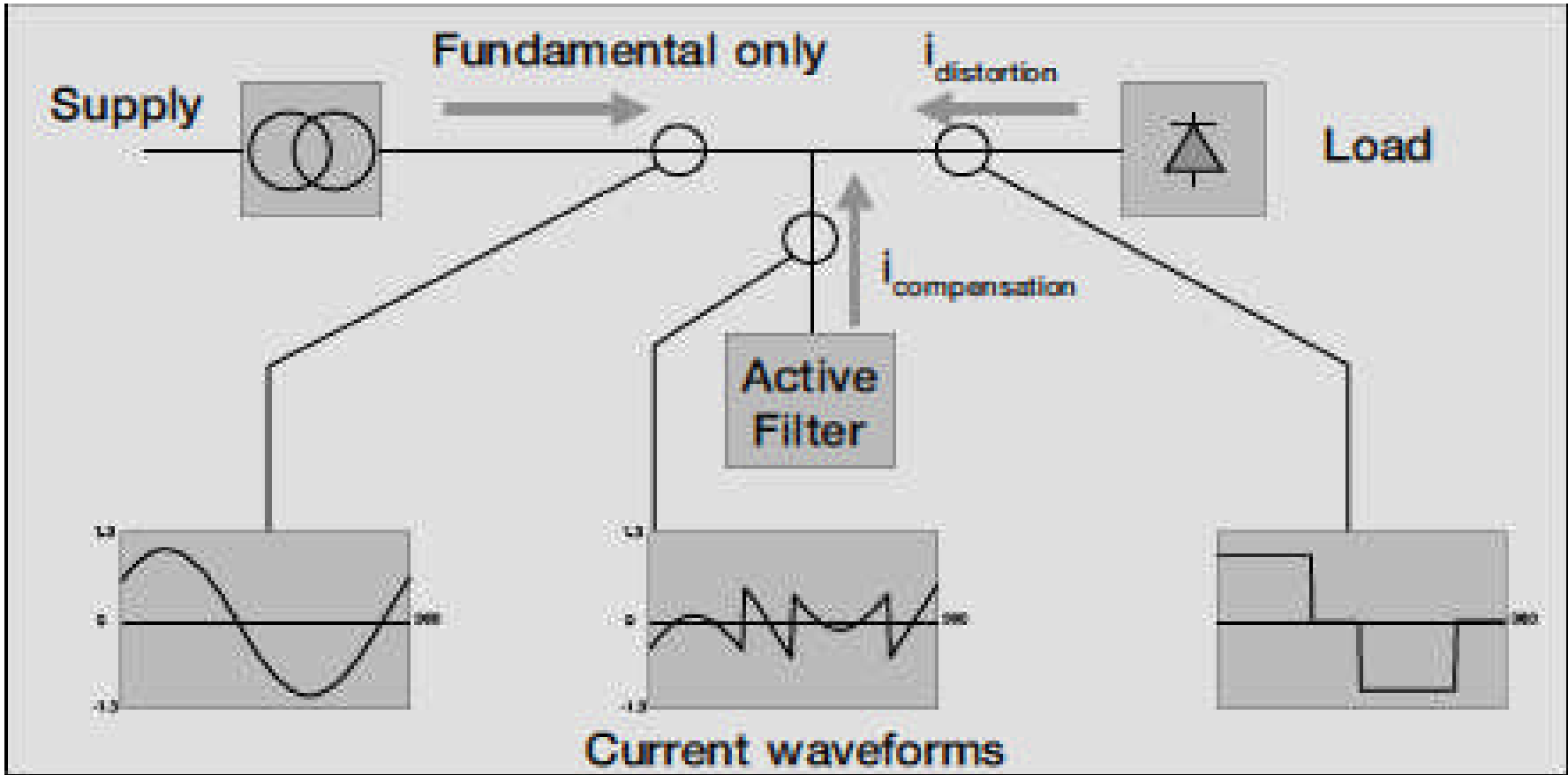

VFD BASIC

Rectifiers design


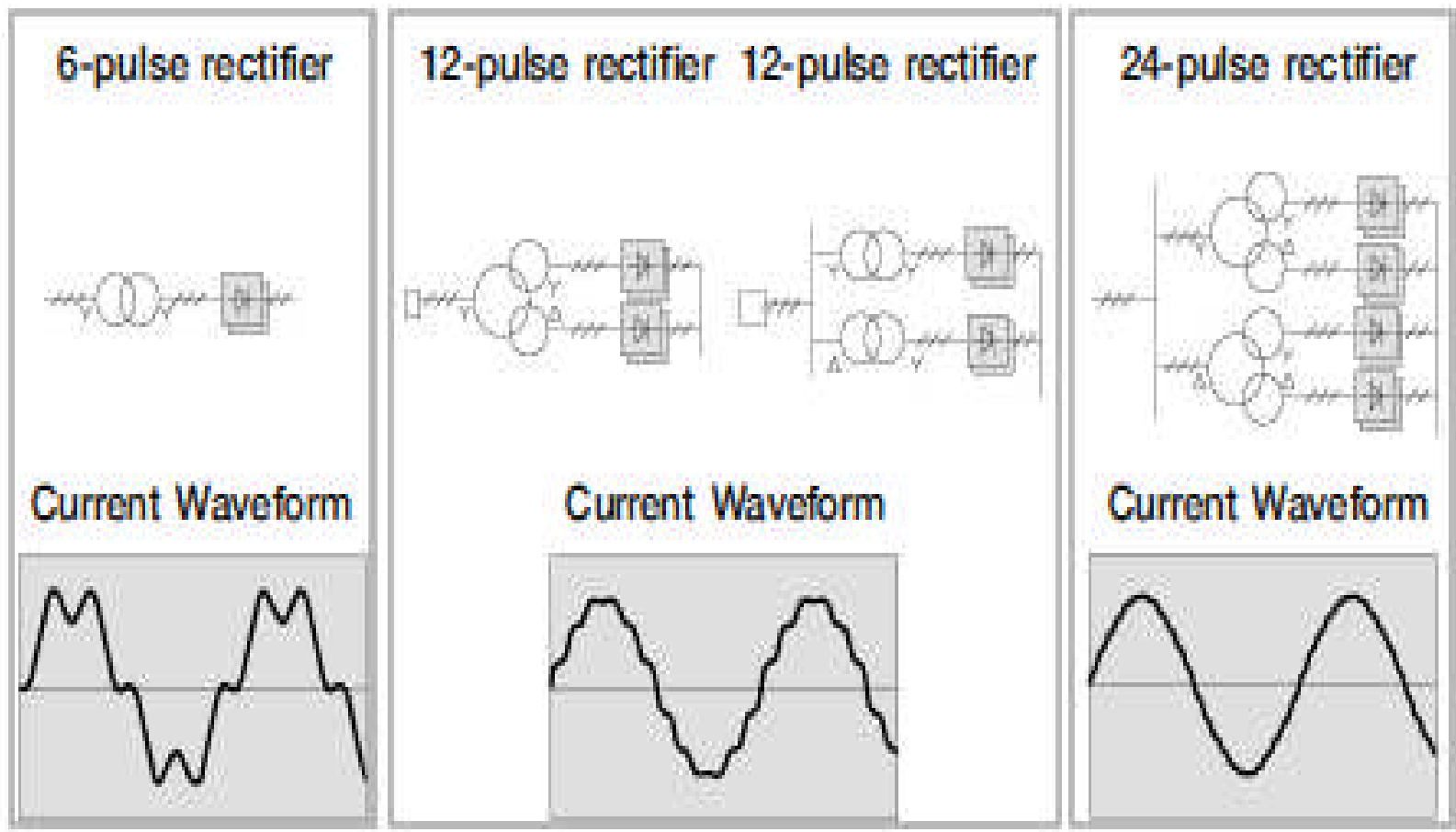


VFD BASIC

Integrated Active Filter



Turn to the Experts™

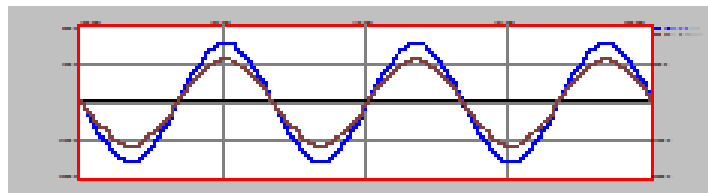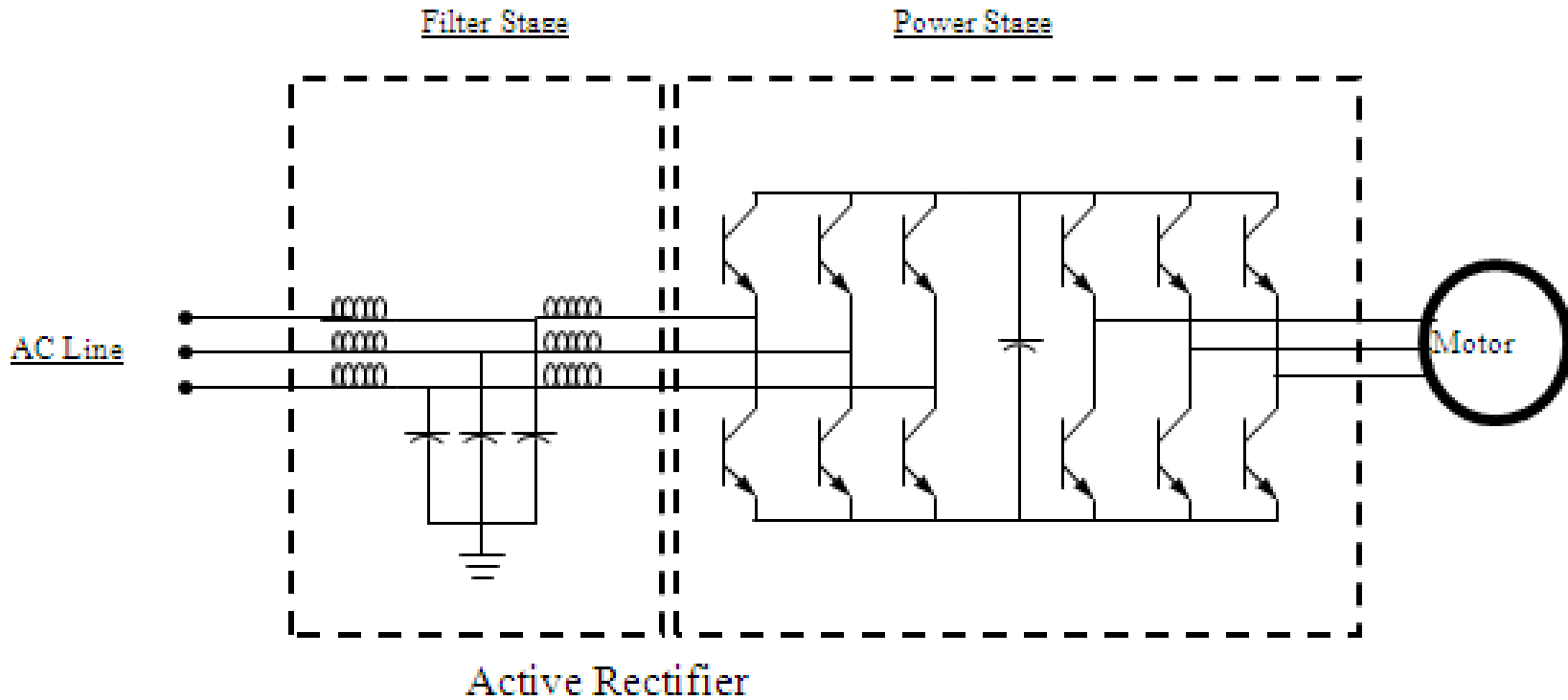

VFD BASIC



Electrical Formulas

Peak Voltage of DC Bus (Non-running) = RMS Voltage X 1.414

Peak Voltage of DC Bus (Running) = RMS Voltage X 1.35

RMS Voltage= Peak Voltage X 0.707

KW (three phase) =
(1.732 X RMS Volt X Amp X Power Factor)/ 1000

HP=1.341 x KW

Ohms Law:

I (current)= E (Voltage)/ R (Resistance) or

R = E / I or

E = R X I

VFD BASIC



Installing VFD with a Generator

What to avoid

- Sizing Generator to load kilowatt rating.
- Flying starts.
- Don't operate the chiller during a transfer of power from the generator power supply to the primary power supply without a closed transition transfer with phase alignment capability

What to do

- Ramp from 0 Hz.
- Keep same Phase Rotation for various power sources
- The calculated load for a VFD starter should be estimated at 2+ times the actual input KW when sizing the generator
- Transfer load in stages